

Lab3			
Project name			
Document ref			
Version			
Release date			
Author	Wu Fei		
Classification	[Document classification]		
Distribution List	[Distribution list]		
Approved by	Name	Signature	Date



Ming Hsieh Department of Electrical Engineering
University of Southern California, Los Angeles, CA 90089
Spring 2022
EE 477

Revision History

[illegible]

CATALOG

1 MOTIVATION	错误!未定义书签。
2 XOR DESIGN	错误!未定义书签。
3 1_BIT FULL ADDER DESIGN	错误!未定义书签。
3.1 DRAW A 1B FULL ADDER SCHEMATIC AS SHOWN.....	错误!未定义书签。
3.2 DESIGN A DELAY MEASUREMENT CIRCUIT	错误!未定义书签。
3.2.1 (A, B, Cin) = (0,1,0) -> (0,1,1). This gives τ_{PLH} for Cout and τ_{PLH} for Sum.	错误!未定义书签。
3.2.2 (A, B, Cin) = (0,1,1) -> (0,1,0). This gives τ_{PLH} for Cout and τ_{PLH} for Sum.	错误!未定义书签。
3.3 DELAY TEST	错误!未定义书签。
3.3.1 P = NAND2_1X, Q = NAND2_1X.....	错误!未定义书签。
3.3.2 P = NAND2_4X, Q = NAND2_1X.....	错误!未定义书签。
3.3.3 P = NAND2_4X, Q = NAND2_4X.....	错误!未定义书签。
3.4 LAYOUT	错误!未定义书签。
4 4_BIT RIPPER CARRY ADDER	错误!未定义书签。
4.1.1 Test the functionality	错误!未定义书签。
4.1.2 Worst part.....	错误!未定义书签。
4.1.3 Layout.....	错误!未定义书签。

1 Motivation

The delay of **RCAs** (Ripple Carry Adders) increases linearly as the number of inputs grows. One of the faster adders is the CSA (Carry Select Adder) which uses parallelism to increase speed with higher area costs. You will design (the layout) of an 8-bit CSA.


- Use **rise and fall time for all input stimuli = 10ps** (Note that it is NOT 100)
- For functionality waveforms, please write what the inputs and expected outputs are for each case. Example: Inputs are A=11111111 (255 in decimal), B=10000000 (128 in decimal), C0=0, expected outputs are C8=1, S=01111111. Then show the 9 output waveforms only.
- The input transition you chose for worst case delay of the CSA.
- Average delays for C8 for schematic and extracted.

2 MUX design

- An N-bit wide, M-to-1 multiplexer (MUX) has M inputs each of which is N-bits. It selects one of them to pass to output (which has N bits). Selection is done using $\log_2 M$ select bits which are inputs.
- Design a 4-bit wide 2-to-1 MUX schematic. It will have 2 sets of inputs, each of which is 4 bits. It will also have a single select bit input and a 4-bit output.
- Design a 2-bit wide 2-to-1 MUX schematic. It will have 2 sets of inputs, each of which is 2 bits. It will also have a single select bit input and a 2-bit output. You only need 2 bit muxes in the CSA design.
- Draw the schematic and layout and verify the functionality

2.1 1bit mux2

Schematic

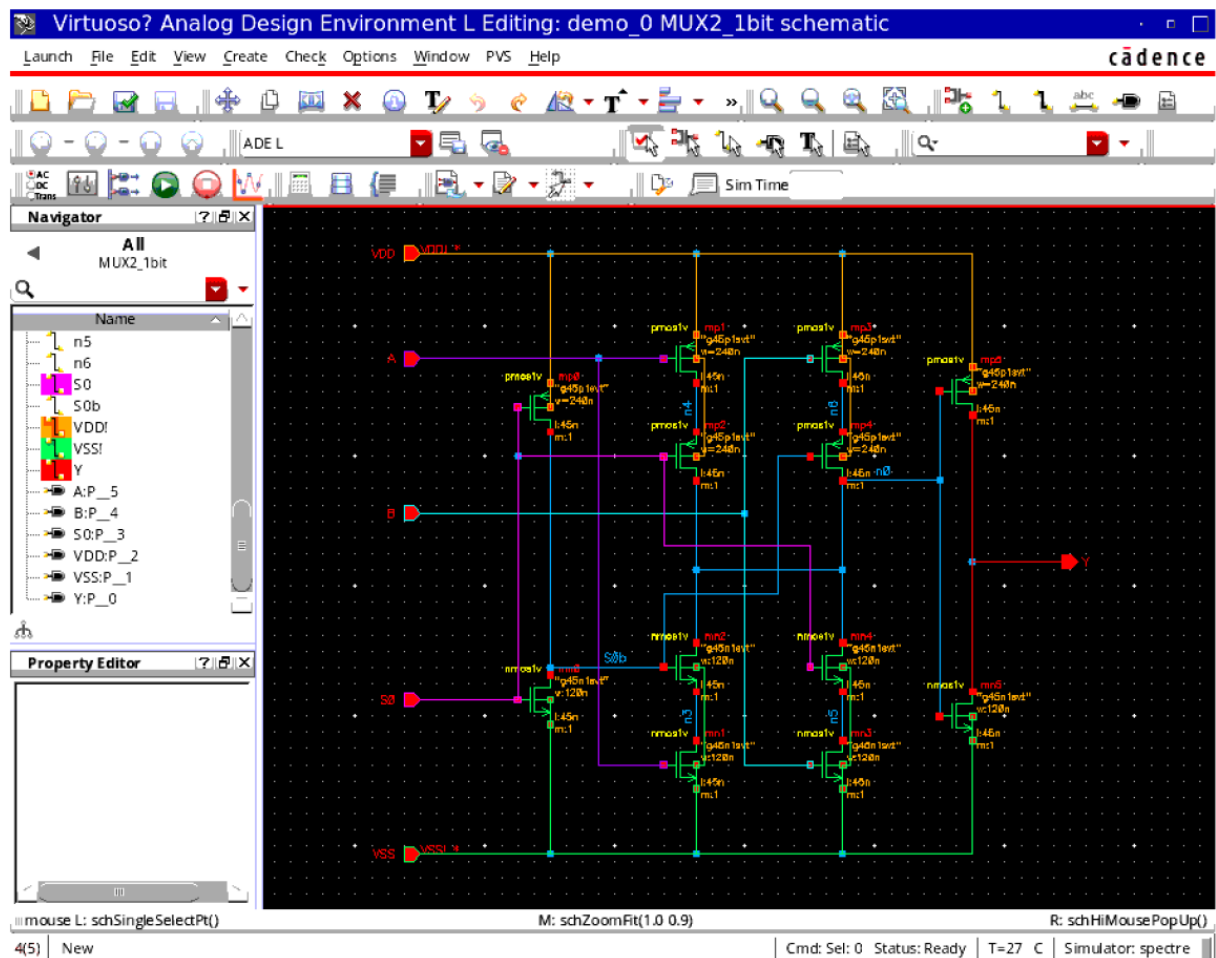

```
w:\fei\g\viternoi-scf2\lab3
radix 1 1 1
vname A B S0
io i i i

tunit 1ns
vih 1
vil 0
voh 1
vol 0
trise 10p
tfall 10p

tdelay 0 0 0 0

;mux PLH for Cout and PHL for Sum

0 0 0 0
1 0 0 1



2 0 1 0
3 0 1 1

4 1 0 0
5 1 0 1


6 1 1 0
7 1 1 1

~
~
~
~

13,14 All
```

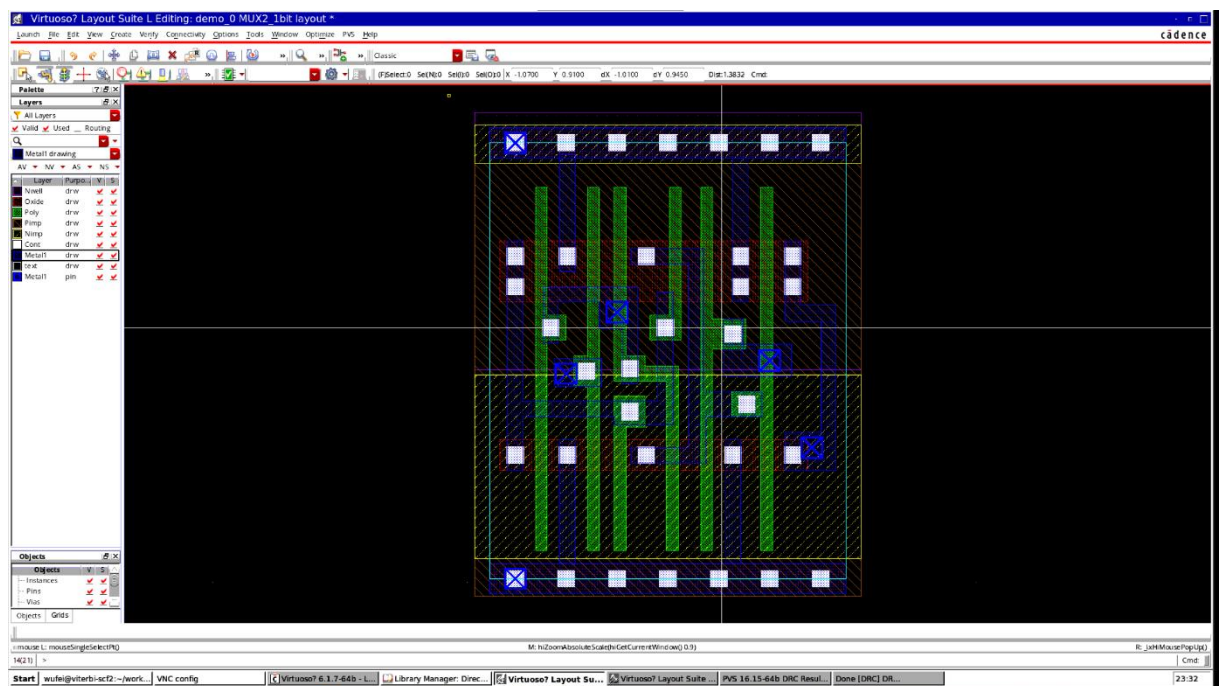 
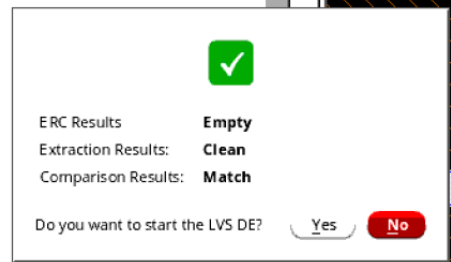
```
#####
#
# Run Result          : MATCH
#
# Run Summary         : [INFO] ERC Results: Empty
#                     : [INFO] Extraction Clean
#
# ERC Summary File    : MUX2_1bit.sum
# Extraction Report File : MUX2_1bit.rep
# Comparison Report File : MUX2_1bit.rep.cls
#
#####
```




```
Total CPU Time          : 1(s)
Total Real Time         : 1(s)
Peak Memory Used        : 26(M)
Total Original Geometry : 71(71)
Total DRC RuleChecks    : 562
Total DRC Results       : 0 (0)
Summary can be found in file MUX2_1bit.sum
ASCII report database is /home/viterbi/03/wufei/work_gpdk045/DRC/MUX2_1bit.drc_error
Checking in all SoftShare licenses.

Design Rule Check Finished Normally. Thu Mar 10 23:31:23 2022
```

2.2 2bits mux

Schematic

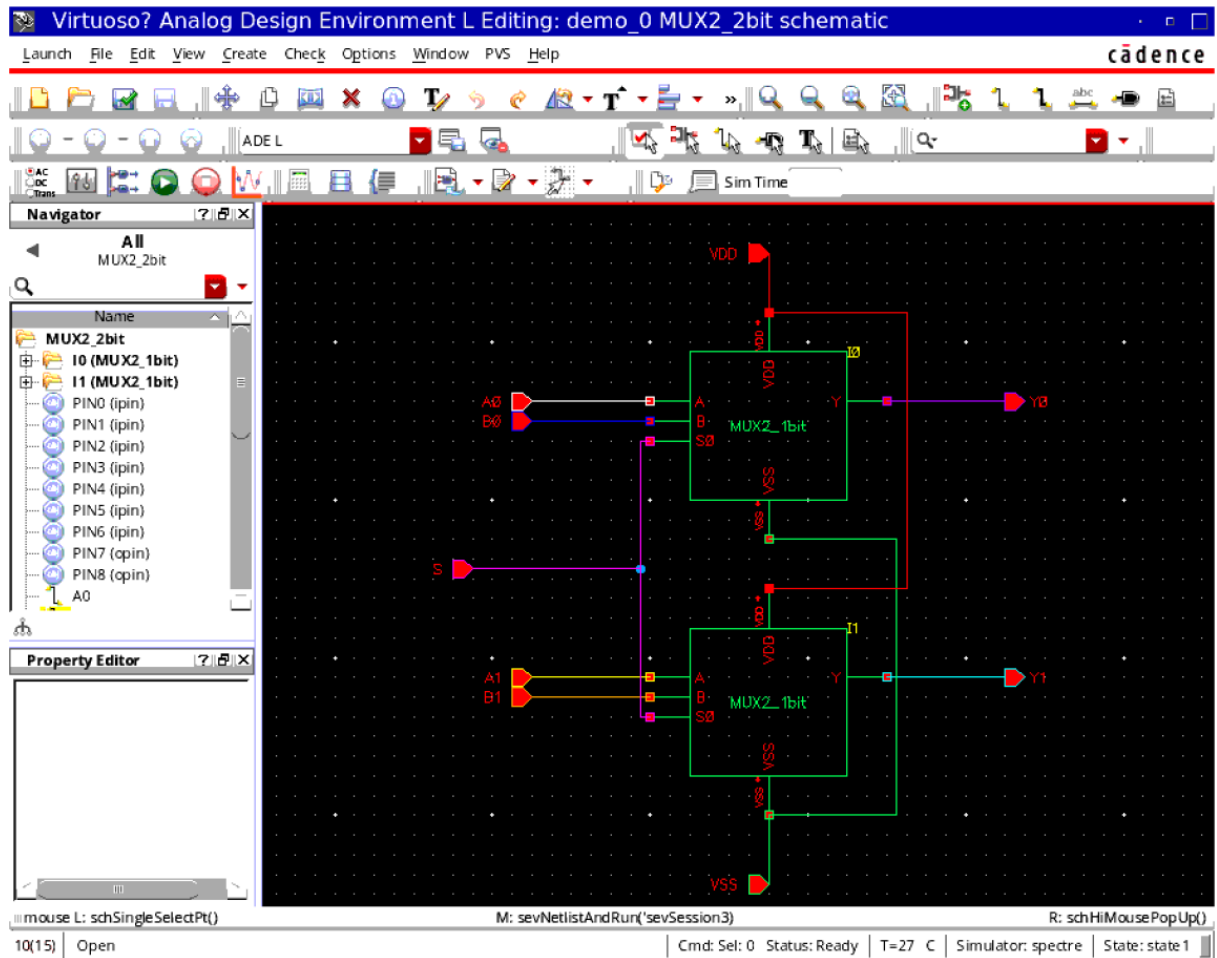

```
wufei@viterbi-scf2:lab3
radix 1 1 1 1 1
vname A1 A0 B1 B0 S
io i i i i i

tunit 1ns
vih 1
vil 0
voh 1
vol 0
trise 10p
tfall 10p

tdelay 0 0 0 0 0 0

;mux PLH for Cout and PHL for Sum

0 0 0 0 0 0
1 1 1 0 0 0


2 1 1 0 0 1
3 1 0 0 1 0

4 1 0 0 1 1
5 0 1 1 0 0

6 0 1 1 0 1
7 1 1 0 0 0

8 1 1 0 0 1

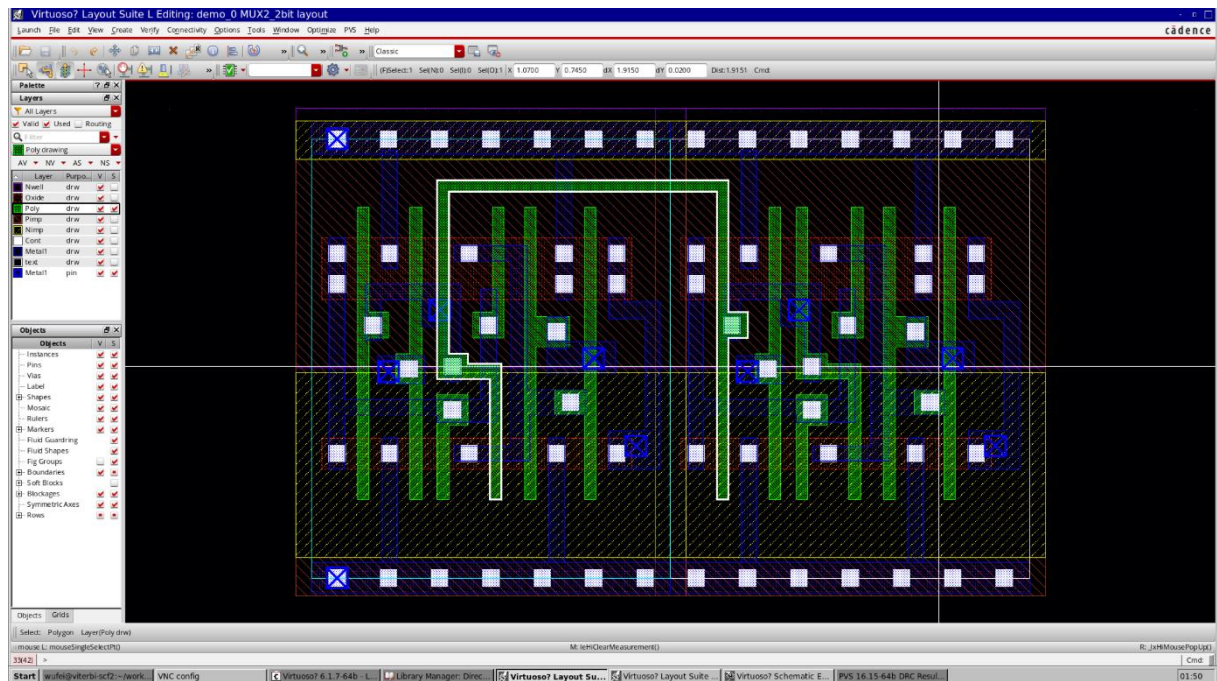~
~
"mux2bit.vec" 31L, 311C written 29,11 All
```



```
#####
#
# Run Result          : MATCH
#
# Run Summary         : [INFO] ERC Results: Empty
#                     : [INFO] Extraction Clean
#
# ERC Summary File    : MUX2_2bit.sum
# Extraction Report File : MUX2_2bit.rep
# Comparison Report File : MUX2_2bit.rep.cls
#
#####
```

Checking in all SoftShare licenses.

PVS Comparison Finished. Fri Mar 11 01:48:05 2022

```
Total CPU Time          : 0(s)
Total Real Time         : 1(s)
Peak Memory Used        : 26(M)
Total Original Geometry : 112(135)
Total DRC RuleChecks    : 562
Total DRC Results       : 0 (0)
Summary can be found in file MUX2_2bit.sum
ASCII report database is /home/viterbi/03/wufei/work_gpd045/DRC/MUX2_2bit.drc_err
Checking in all SoftShare licenses.
```


Design Rule Check Finished Normally. Fri Mar 11 01:50:41 2022

3 8_bit carry select adder design

- A CSA computes the outputs for the later stages, i.e., the one processing the higher significant bits, for two cases of input carry as 1 and also as 0, both, while the earlier stages work on the addition of lower significant bits. By the time, the actual carry bit is calculated by the earlier stages, the higher stages are also done and all it takes to produce the complete result is to use the multiplexer to pass the correct results.
- You may choose any of the circuit recommendations presented during lecture and discussion classes.
- You are welcome to use your 4-bit RCA of lab2 as part of this lab.
- Do a functionality test. Use at least 3 different combinations for $\langle a[8:1], b[8:1], c0 \rangle$.
- Build a delay measurement circuit. All inputs $\langle a[8:1], b[8:1], c0 \rangle$ should be applied through INV_1X. Connect an INV_4X for each output (i.e., $\langle c8, s[8:1] \rangle$).
 $\langle c8, s[8:1] \rangle \leftarrow \langle a[8:1], b[8:1], c0 \rangle$
- Find an input transition which results in worst case delay for output C8. Repeat for S8.
- For this input transition, measure the average delay.
- Draw the layout for the 8-bit CSA.
- Draw layout for the delay measurement circuit and measure average delay of C8 on the extracted view using the same worst case input transition.

3.1 CSA_8bit

3.1.1 SCH

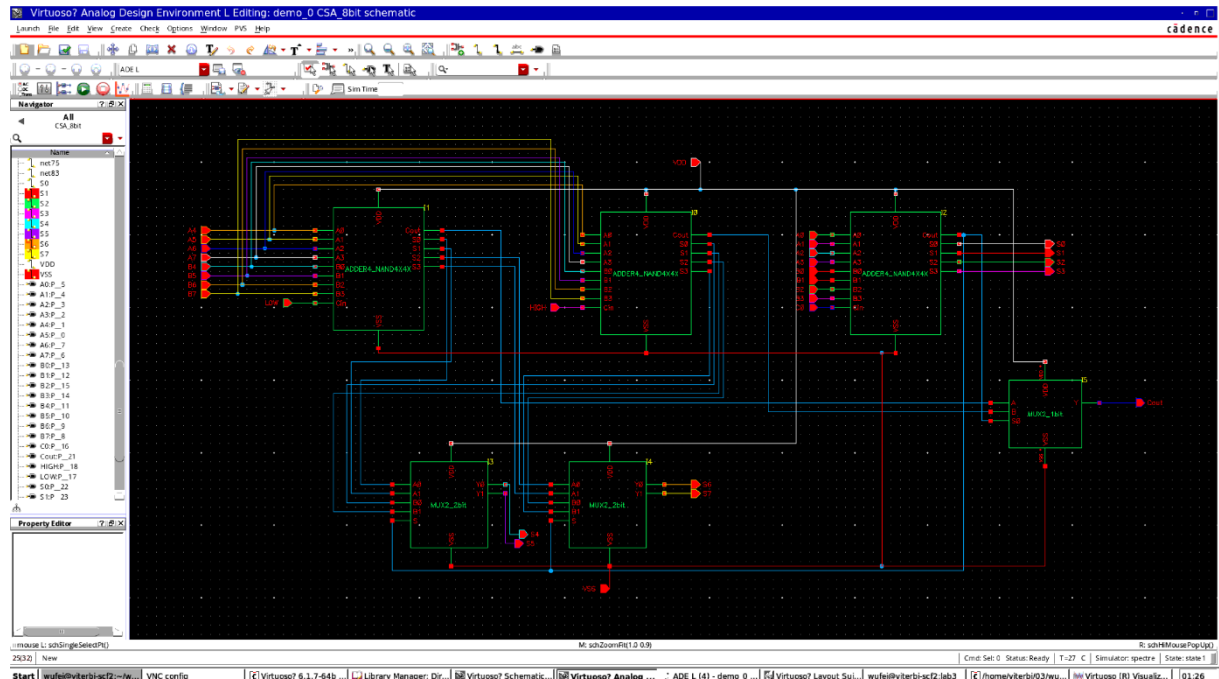

```
wu:feigviterbi-scf2:lap?
radix 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1
vname A7 A6 A5 A4 A3 A2 A1 A0 B7 B6 B5 B4 B3 B2 B1 B0 C0
io i i i i i i i i i i i i i i i i


tunit 1ns
vih 1
vil 0
voh 1
vol 0
trise 10p
tfall 10p

tdelay 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0


;ADDER PLH for Cout and PHL for Sum
0 0 0 0 0 0 0 0 0 1 1 1 1 1 1 1 1 0
1 0 0 0 0 0 0 0 0 1 1 1 1 1 1 1 1 1

2 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1
3 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 0

4 1 0 1 0 1 0 1 0 0 1 0 1 0 1 0 1 0
```

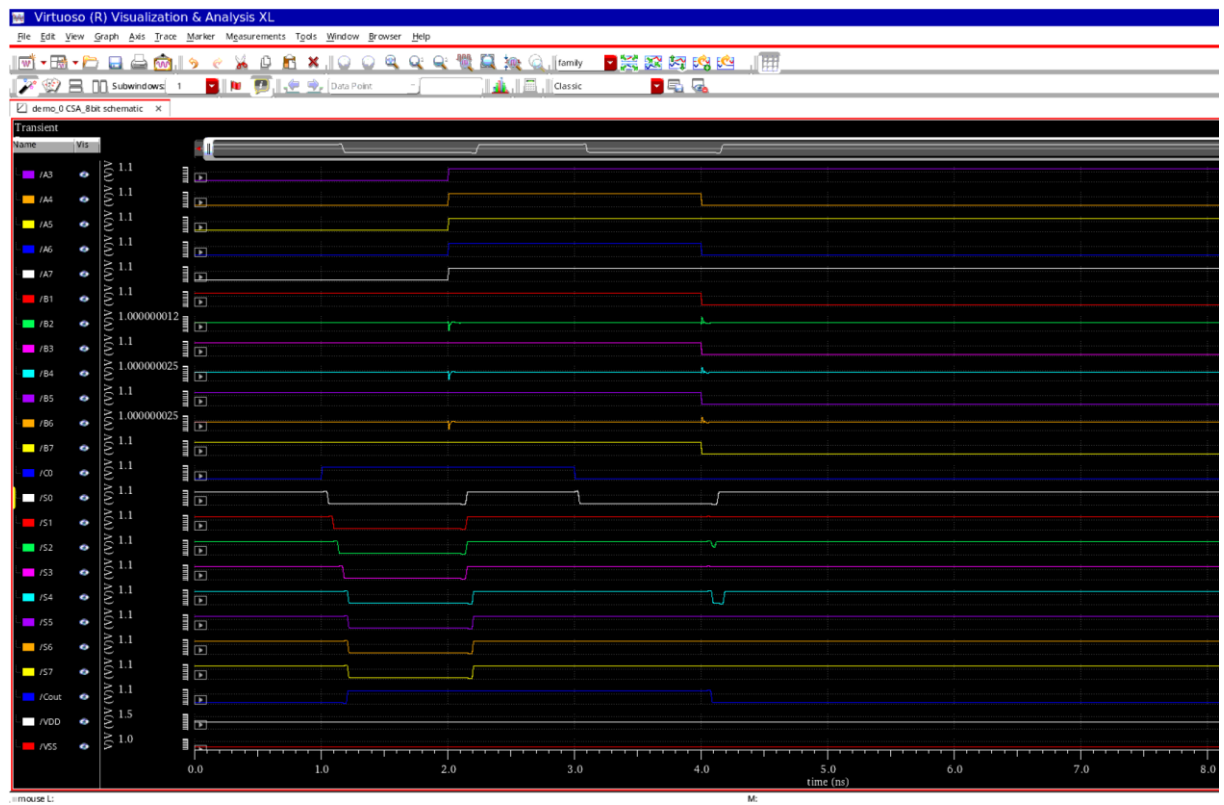

3.2 TEST

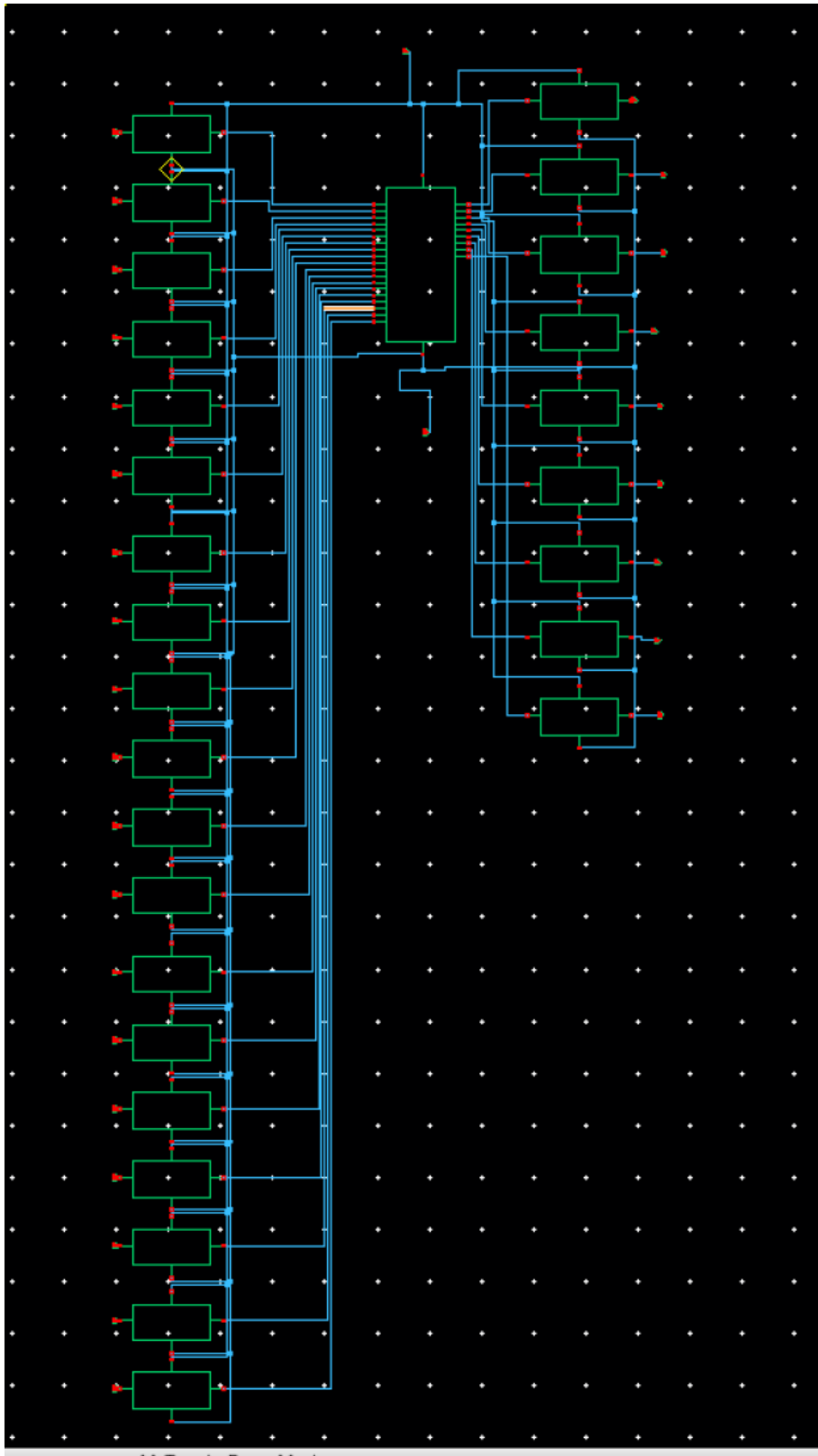


```

wufei@viterbi-scf2:lab3
radix 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1
vname A7 A6 A5 A4 A3 A2 A1 A0 B7 B6 B5 B4 B3 B2 B1 B0 C0
io i i i i i i i i i i i i i i i i

tunit 1ns
vih 1
vil 0
voh 1
vol 0
trise 10p
tfall 10p

tdelay 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0

;ADDER PLH for Cout and PHL for Sum

0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0
1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1

```

delay

Signal1

VT("/Cout")

Signal2

VT("/C0")

Threshold Value 1

0.5

Threshold Value 2

0.5

Edge Number 1

1

Edge Number 2

1

Edge Type 1

falling

Edge Type 2

falling

Periodicity 1

1

Periodicity 2

1

OK

Apply

Defaults

Help

Close

Function Panel

Expression Editor

Selected Output

Name (opt.)

DELAY_Cout

Expression

h2 1 ?td2 nil ?stop nil ?multiple nil

From Design

Calculator

Open

Get Expression

Close

Will be

☒ Plotted/Evaluated

Add

Delete

Change

Next

New Expression

Table Of Outputs


	Name/Signal/Expr	Value	Plot	Save Option
9	B0		yes	allv
10	B1		yes	allv
11	B2		yes	allv
12	B3		yes	allv
13	B4		yes	allv
14	B5		yes	allv

OK


Cancel

Apply

Help

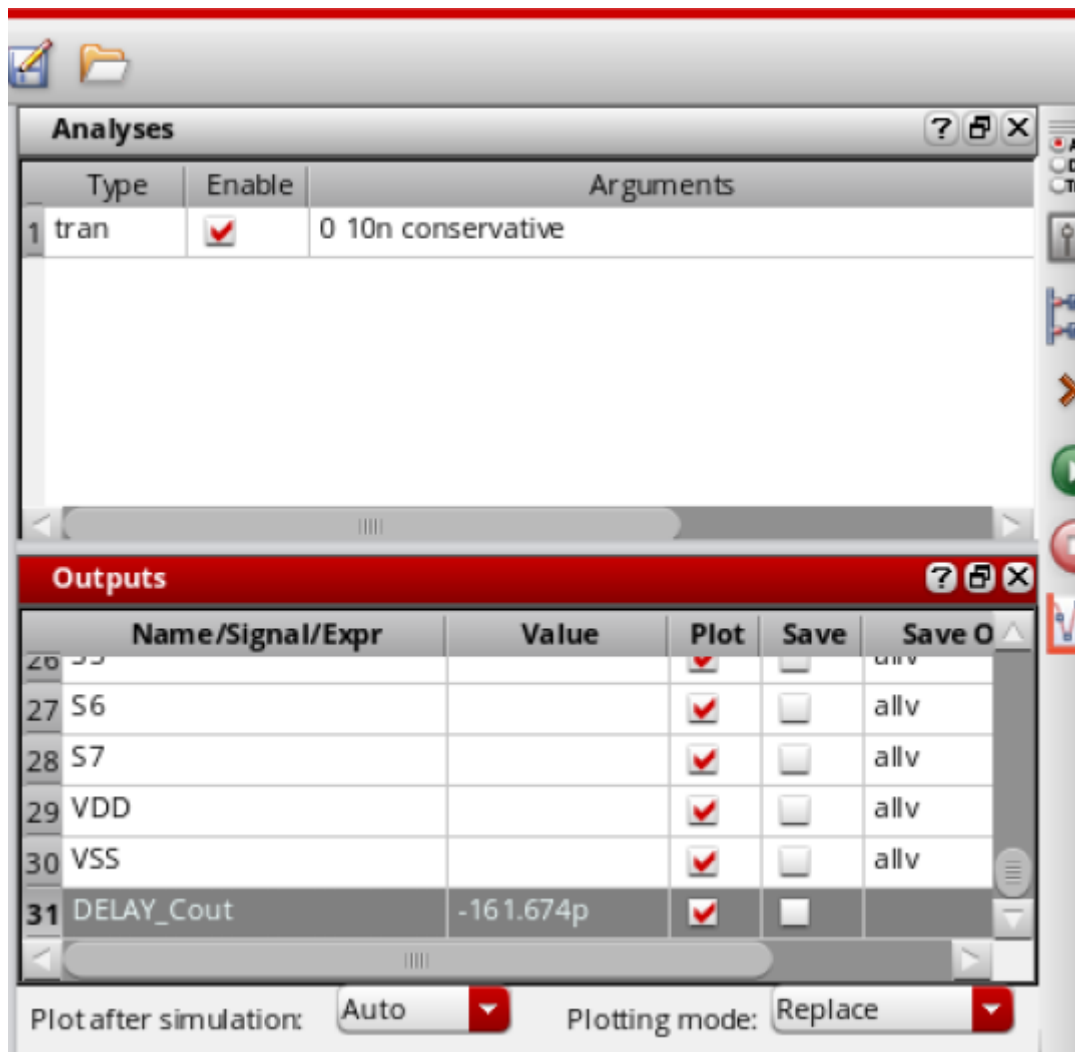

3.3 LAYOUT

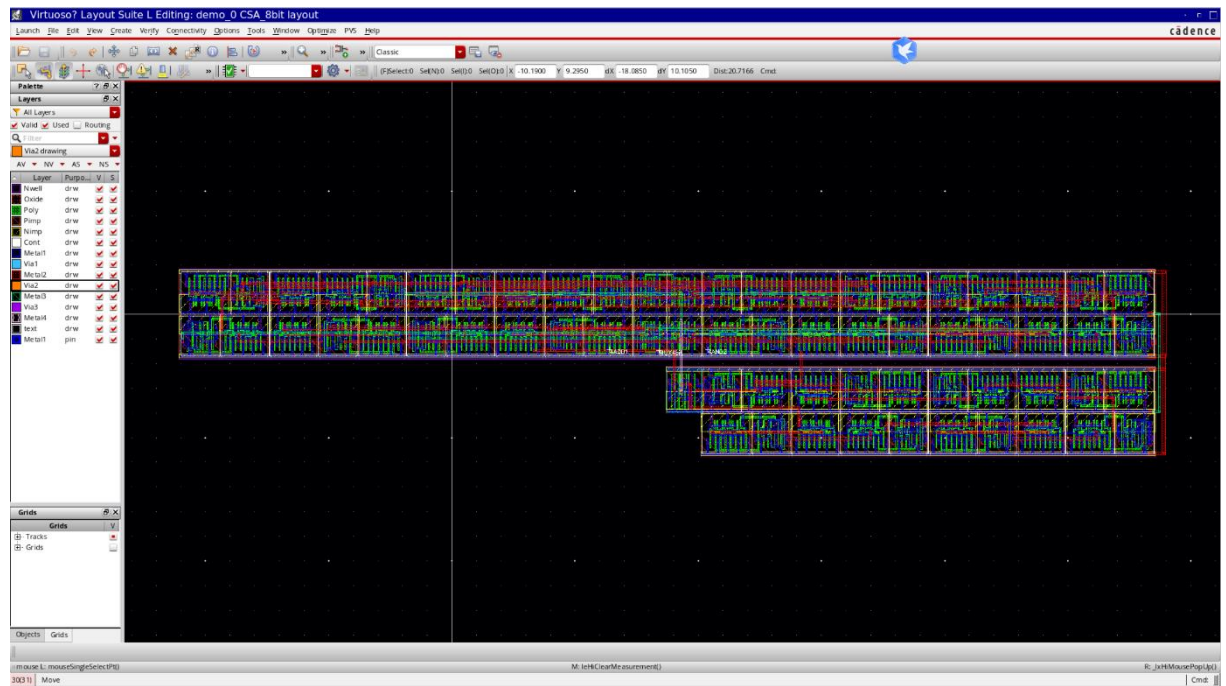

```
#####
#
# Run Result : MATCH
#
# Run Summary : [INFO] ERC Results: Empty
# : [INFO] Extraction Clean
#
# ERC Summary File : CSA_8bit.sum
# Extraction Report File : CSA_8bit.rep
# Comparison Report File : CSA_8bit.rep.cls
#
#####
```

```
#####
Total CPU Time : 2(s)
Total Real Time : 2(s)
Peak Memory Used : 114(M)
Total Original Geometry : 3321(5105)
Total DRC RuleChecks : 562
Total DRC Results : 0 (0)
Summary can be found in file CSA_8bit.sum
ASCII report database is /home/viterbi/03/wufei/work_gpkg045/DRC/CSA_8bit.drc_error
Checking in all SoftShare licenses.
#####
```