

Cadence Virtuoso Tutorial

version 6.2

EE477/577A Nazarian

University of Southern California

Last Update: August 2021

Table of Contents

Cadence Virtuoso Setup	3
Basic Design Flow	5
1. Overall design flow	5
2. Create Library	6
3. Schematic	8
A. Create a cell view	8
B. Draw a schematic	9
4. Run Spectre simulation (Transient analysis)	16
A. Launch ADE (Analog Design Environment) L	16
B. Basic setup	17
C. Model Libraries	17
D. Simuli	18
E. Choose a type of analysis - transient	20
F. Select signals to plot	21
G. Run simulation	21
H. Measurement	22
5. Run Spectre simulation (DC analysis)	25
A. Voltage Source	25
B. Replace Input Pin	26
C. Choosing Analyses	26
D. Run Simulation	27
6. Layout	29
A. Create a layout	29
B. Add an instance - nmos	30
C. Add more instances – pmos, ptap, ntap, and m1_ploy	31
D. Draw metal1	32
E. Run DRC	33
F. Add pins	35
G. Extract	37
H. Run LVS	38
I. Run Spectre simulation	39


Cadence Virtuoso Setup

- A. Please use the steps (in the Cadence Virtuoso Setup Guide, which is separately provided) to be able to run Virtuoso on your account.
- B. Type **virtuoso &** at the command prompt. The “&” is for background execution, it is useful when we want to keep the command prompt in the same console.

Basic Design Flow

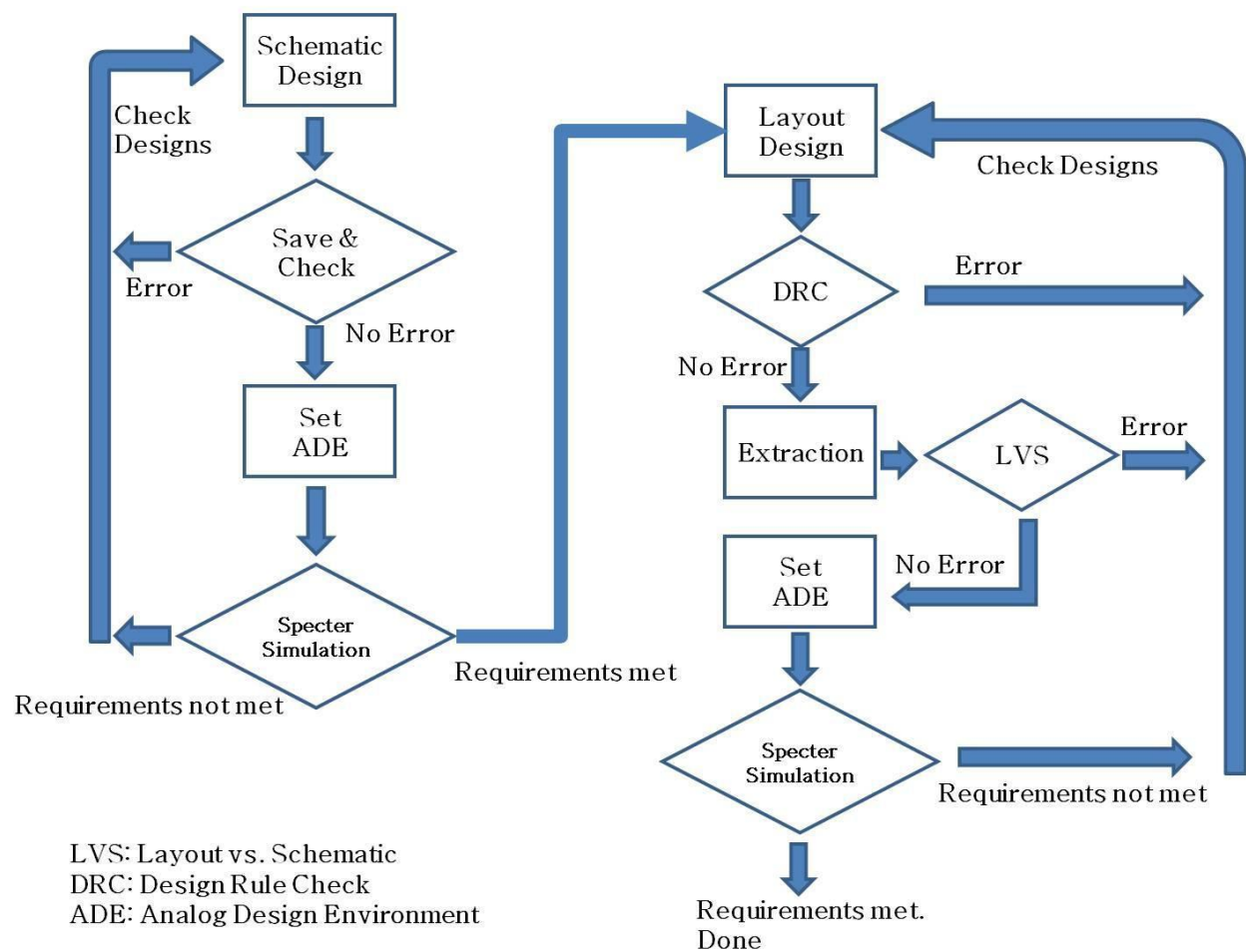
1. Overall design flow

Following flow chart shows overall design flow.




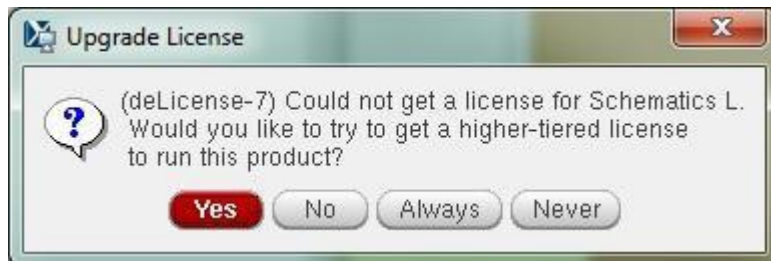2. Create Library


For prompt to access for higher tiered license, click “always”.






A. Tools → Library Manager

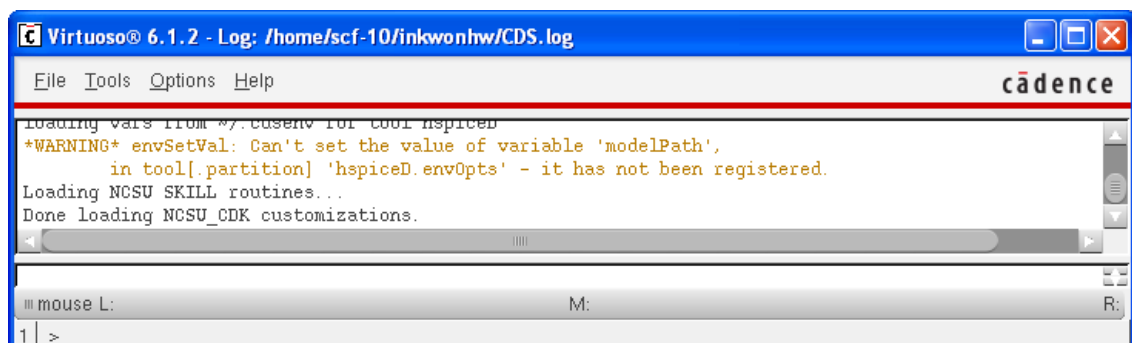

B. File → New → Library

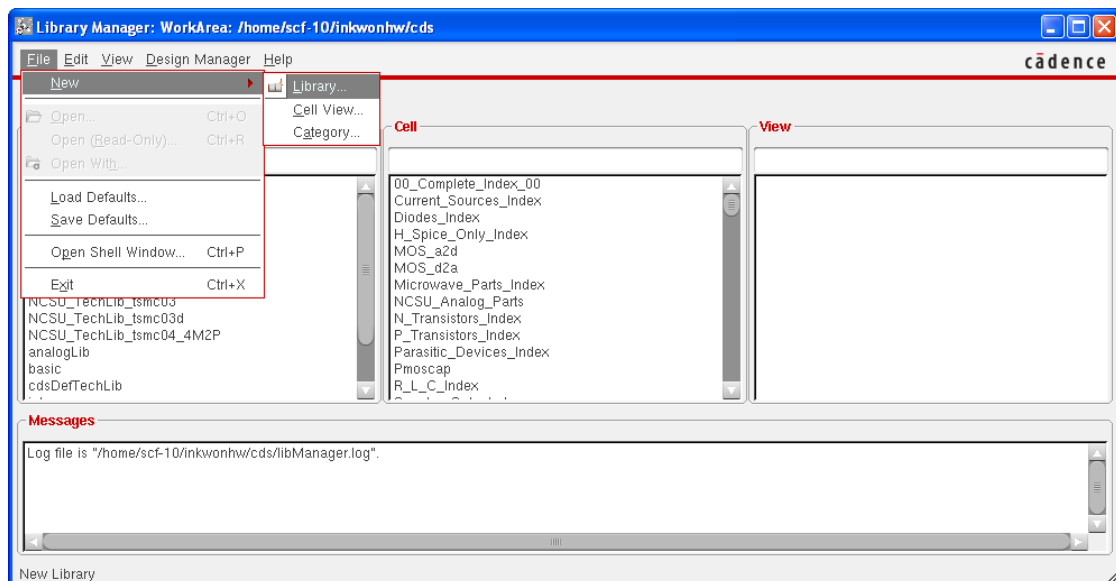

 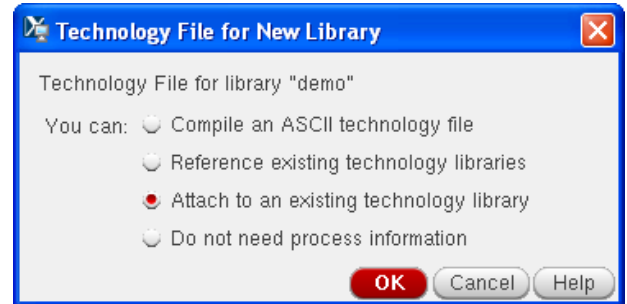
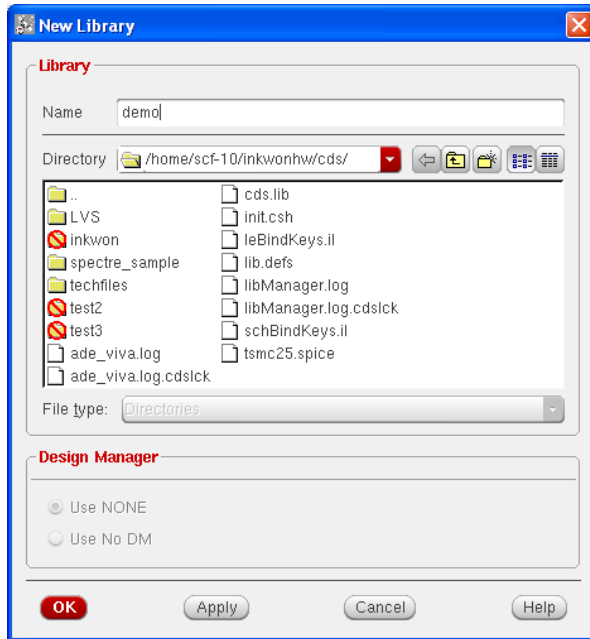
C. Give a name and attach it to a technology library



3. Schematic

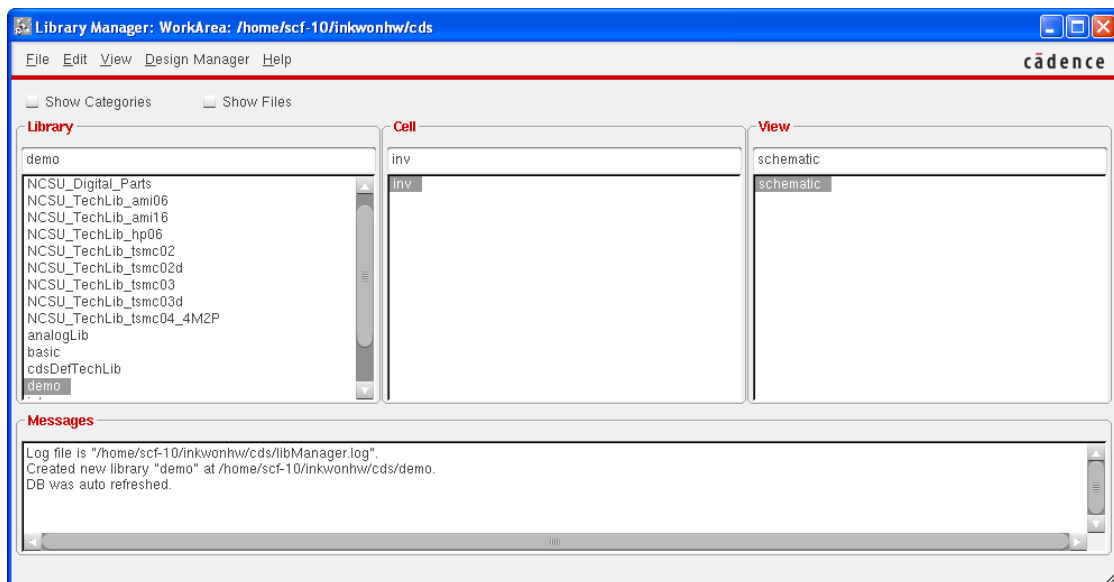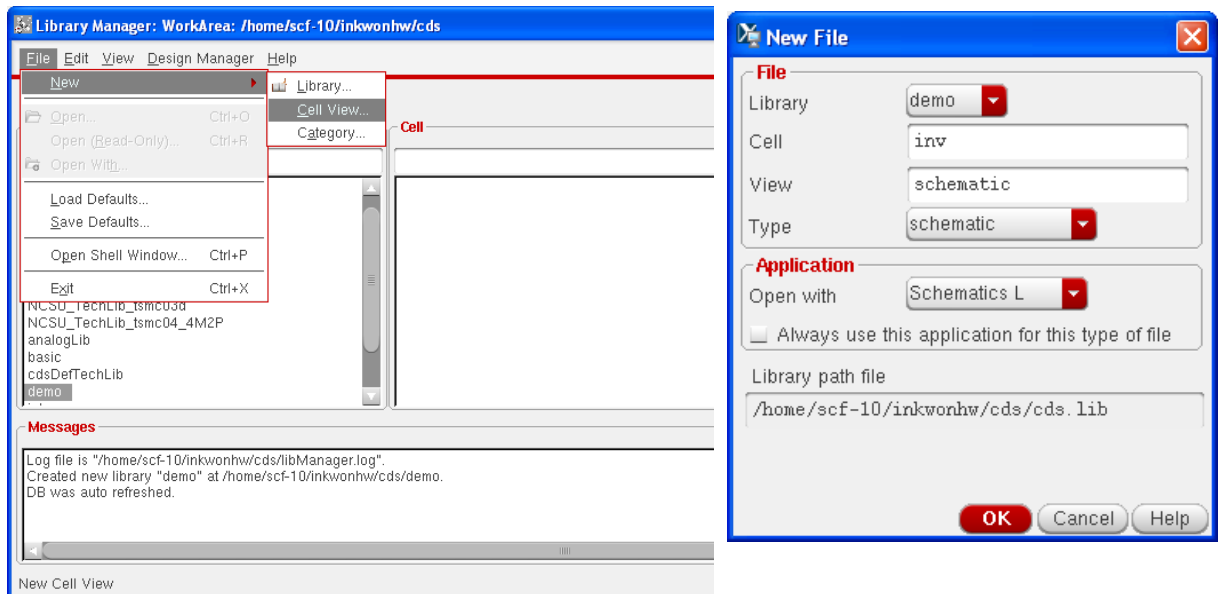A. Create a cell view

select the library just created, File->new







B. Draw a schematic

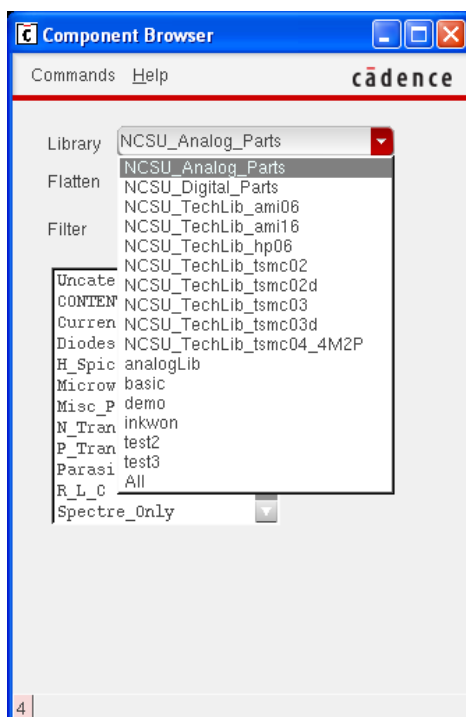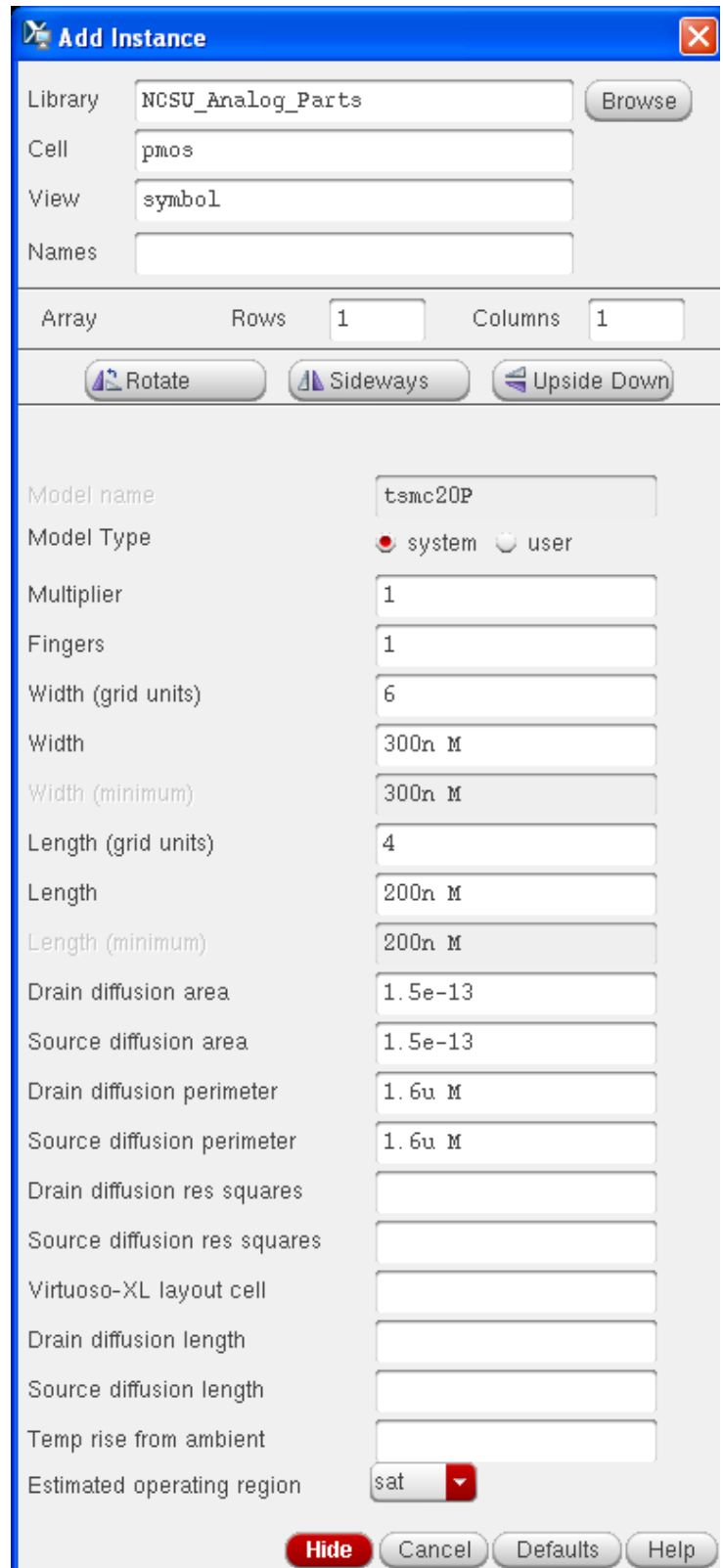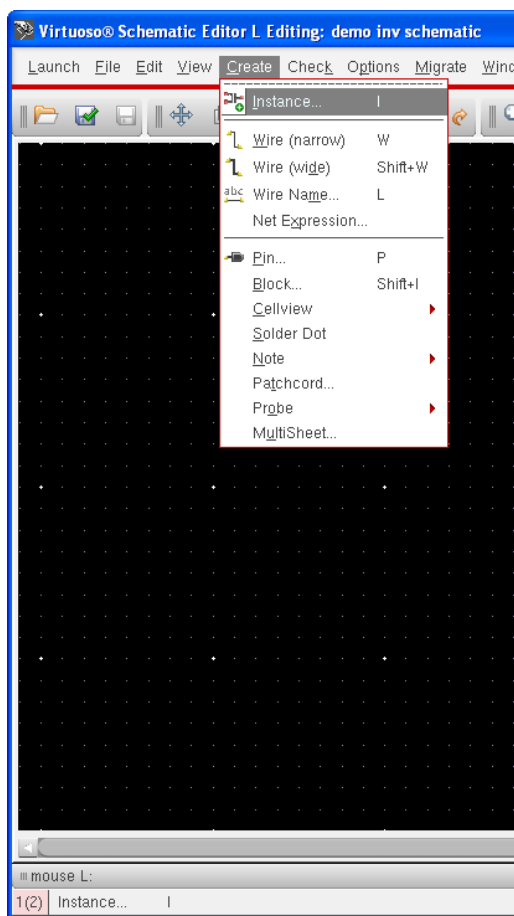i. Add instances – pmos


You can modify Width of transistors. Don't modify length unless you have a special purpose.

You should select a NCSU_Analog_Parts library.





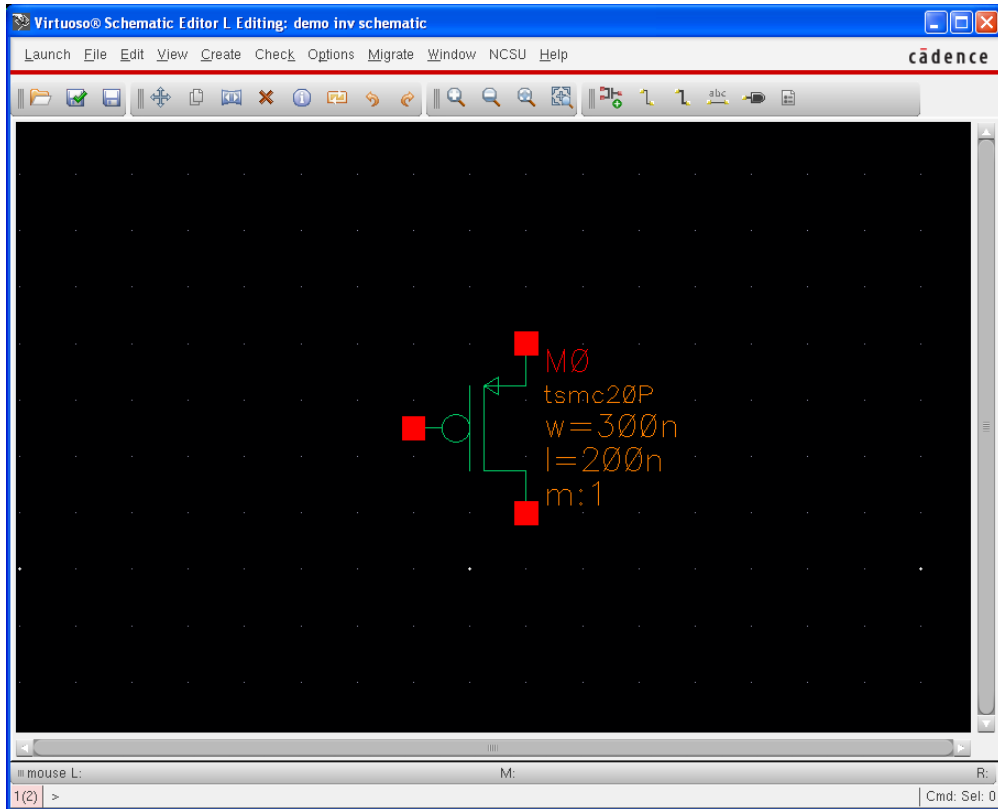


ii. Add instances – nmos, vdd, and gnd

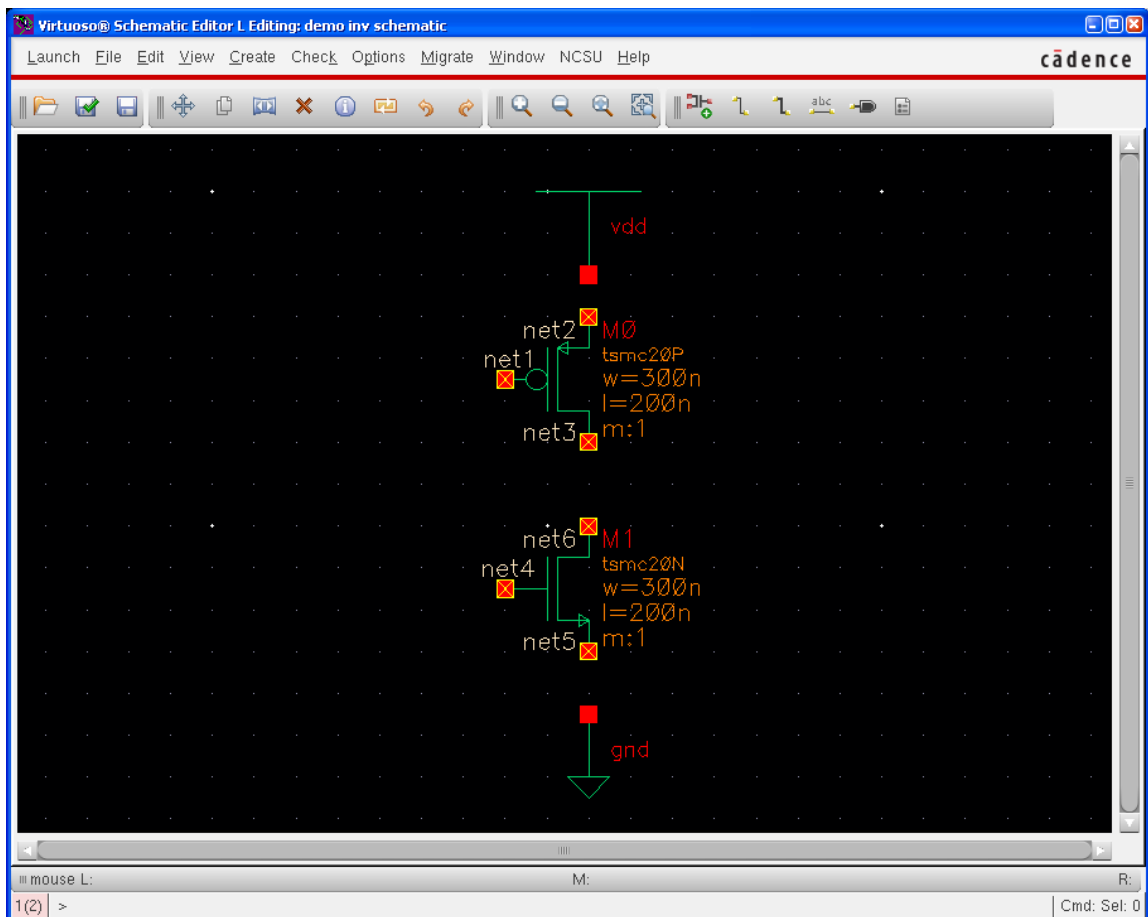


iii. Add wires: Create → Wire

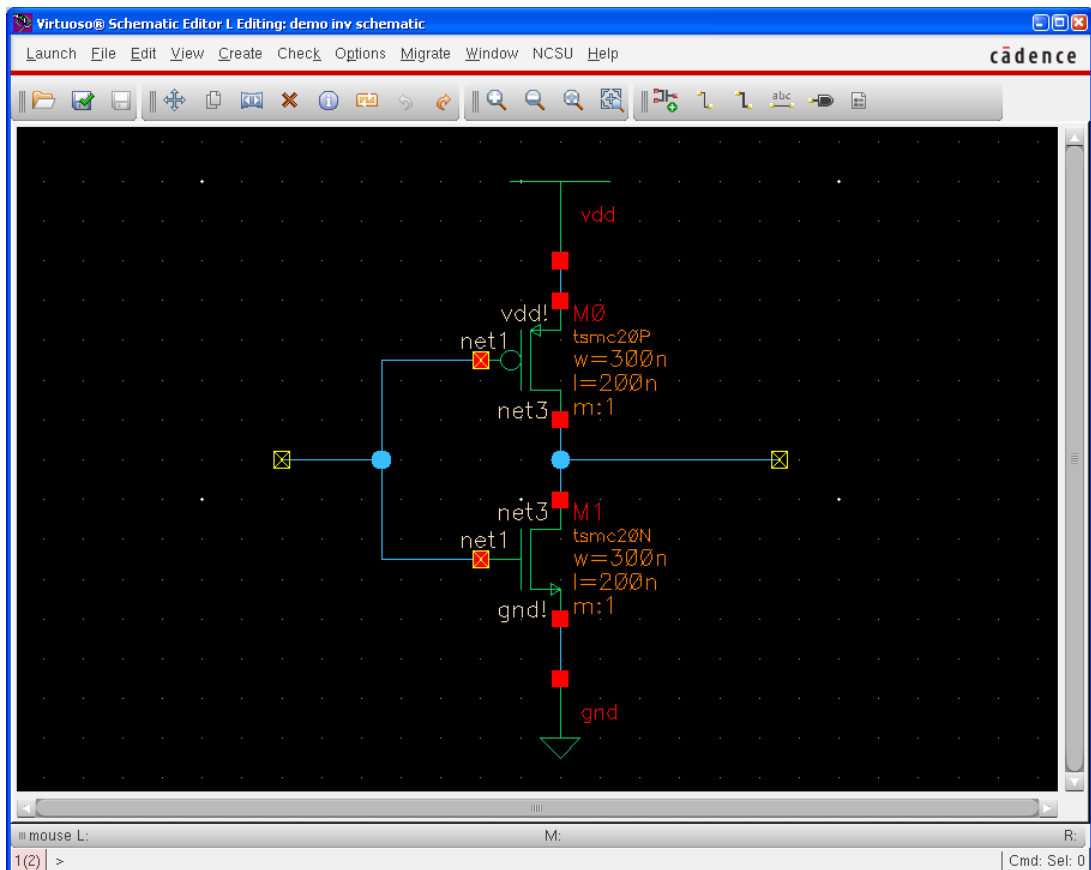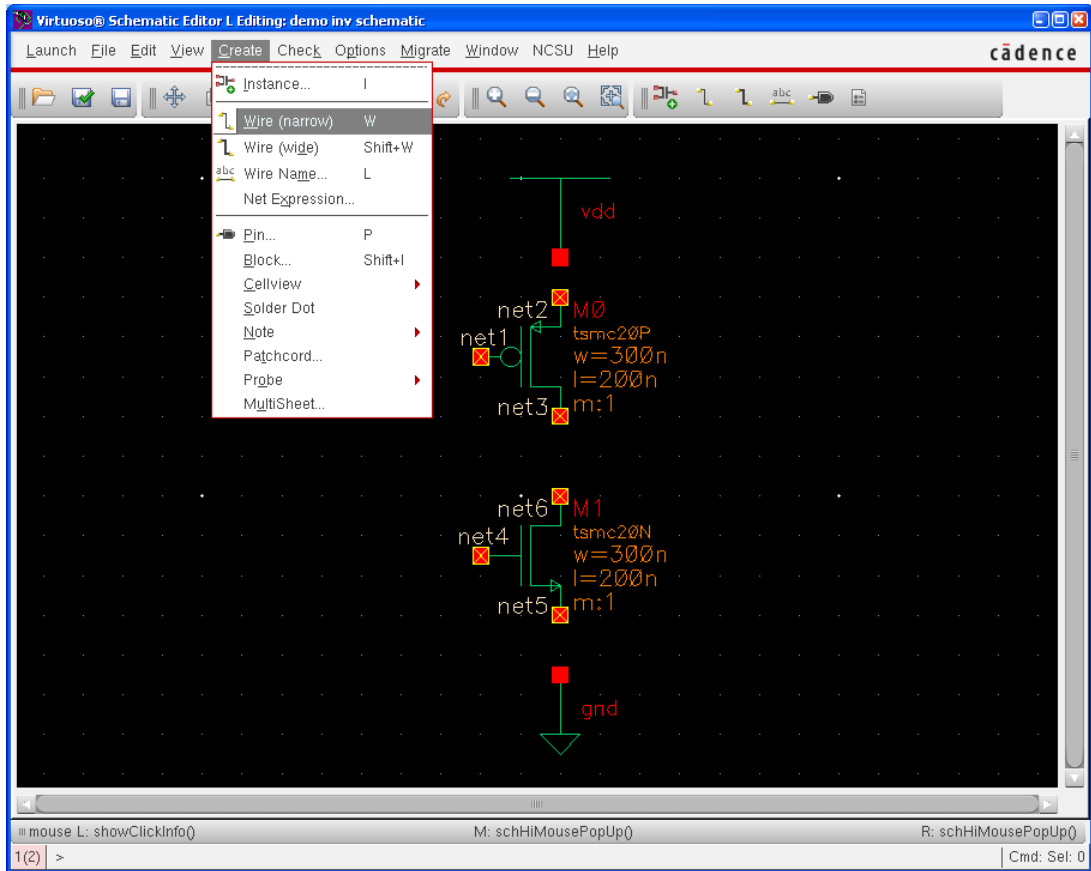



iv. Add pins: Create → Pin

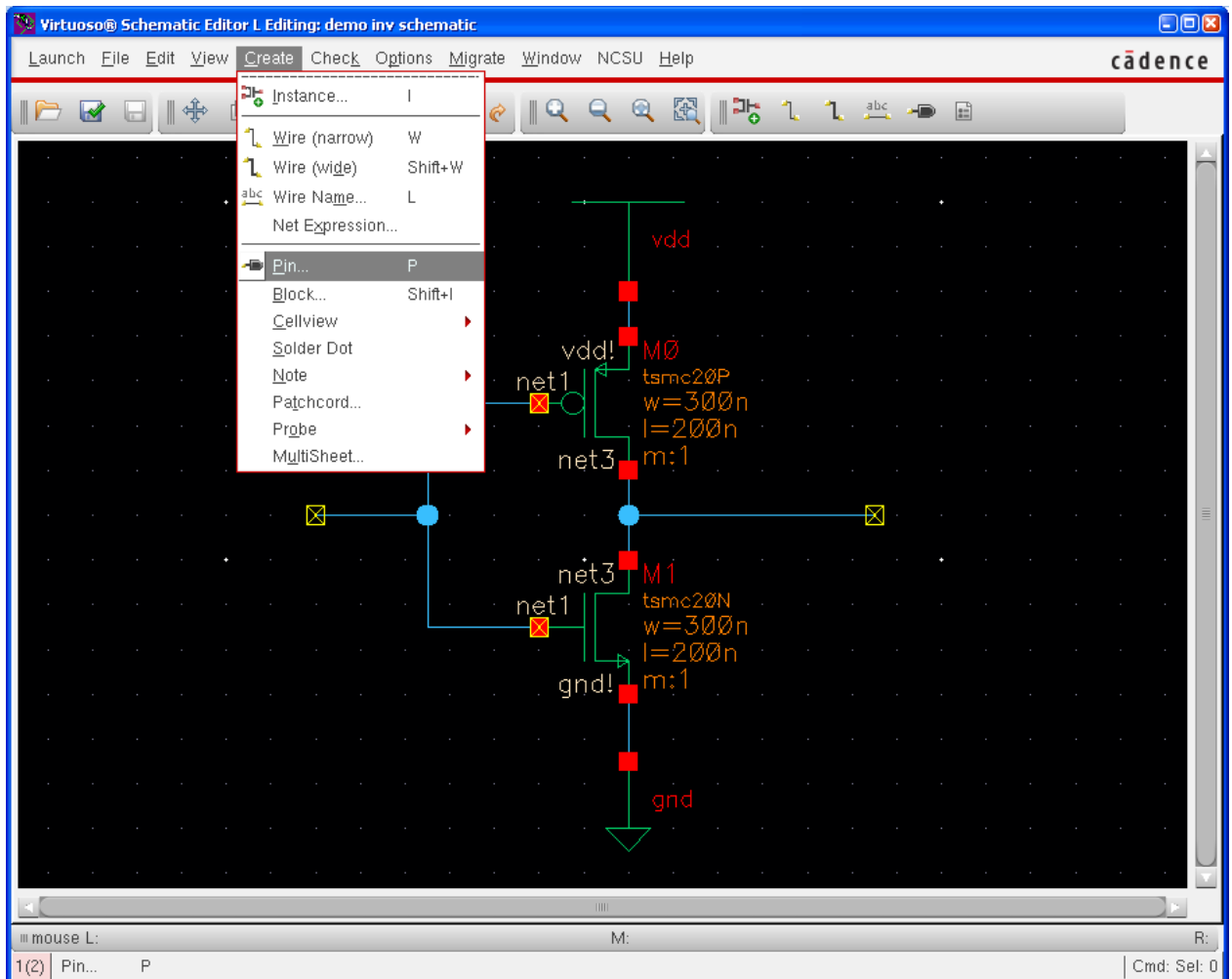

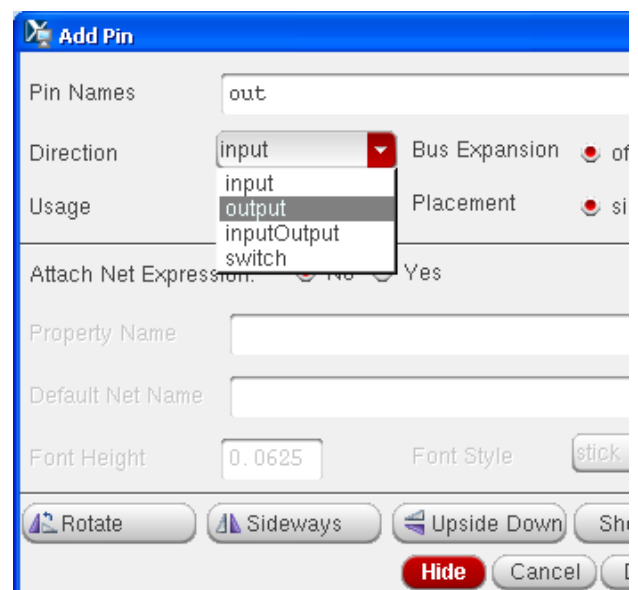We have for different types of direction. For schematics, we only use two types, input and output. InputOutput type is for supply changes, and it is necessary only for layout. We will discuss about this later.



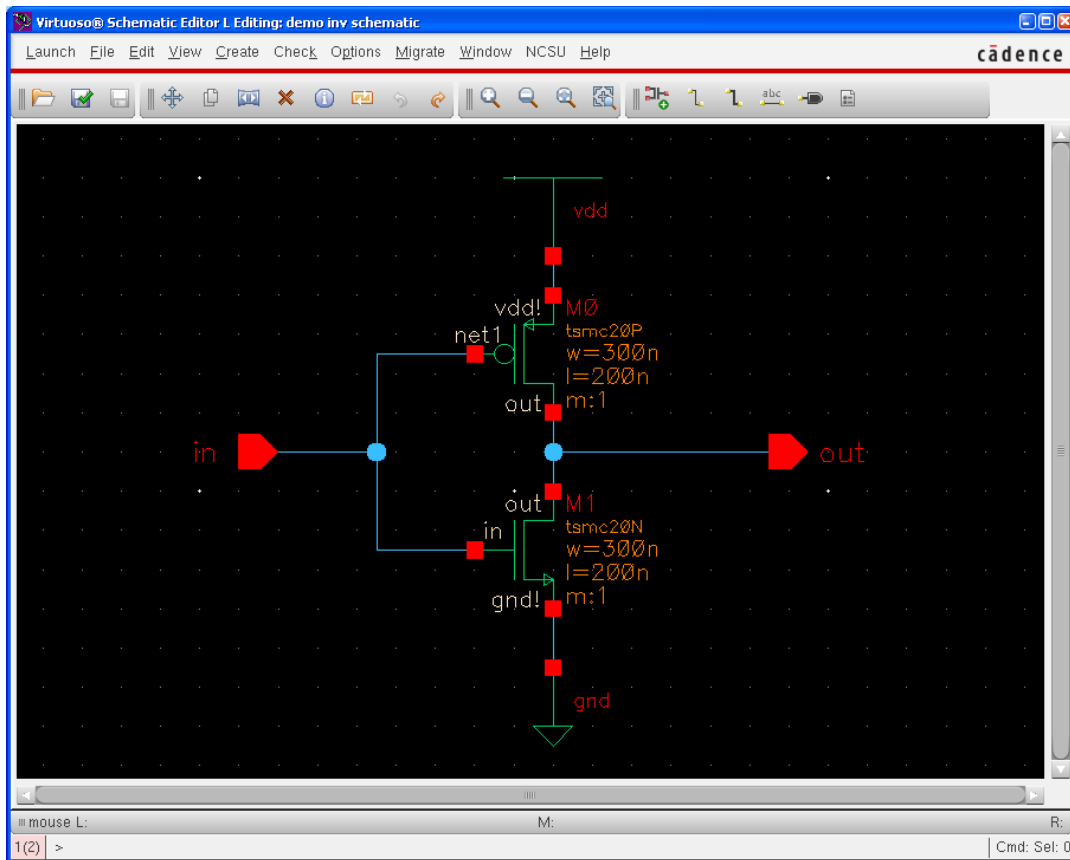


Check and save →  to make sure there are no errors.

Now, we completed a schematic design.

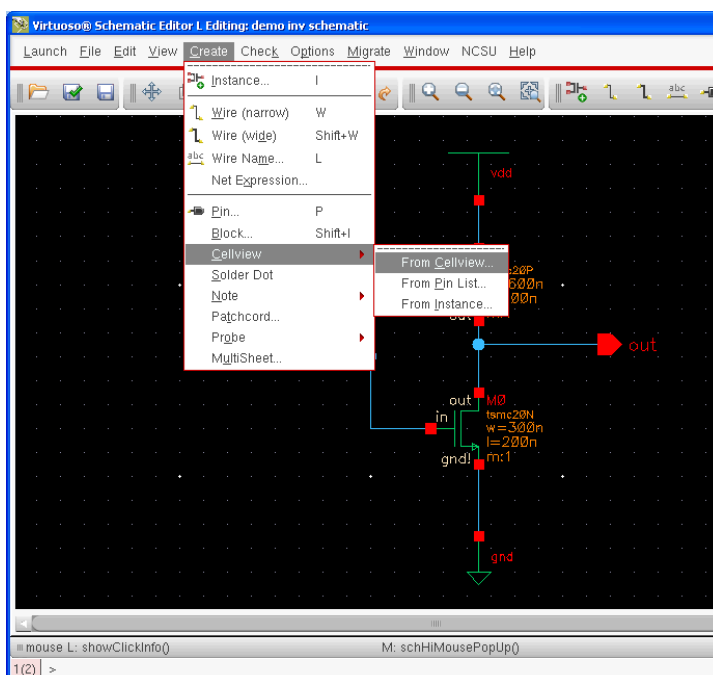C. Create a symbol (Optional)

For hierarchical design, we may need to make symbols of designed circuits.



Create → CellView → From Cellview

Cellview From Cellview

Library Name: Browse

Cell Name:

From View Name: To View Name:

Tool / Data Type:

Display Cellview: ☒

Edit Options: ☒

OK Cancel Defaults Apply Help

Symbol Generation Options

Library Name: Cell Name: View Name:

Pin Specifications


Left Pins	<input type="text" value="in"/>	List
Right Pins	<input type="text" value="out"/>	List
Top Pins	<input type="text"/>	List
Bottom Pins	<input type="text"/>	List


Exclude Inherited Connection Pins:

☒ None ☐ All ☐ Only these:

Load/Save: ☐ Edit Attributes: ☐ Edit Labels: ☐ Edit Properties: ☐

OK Cancel Apply Help

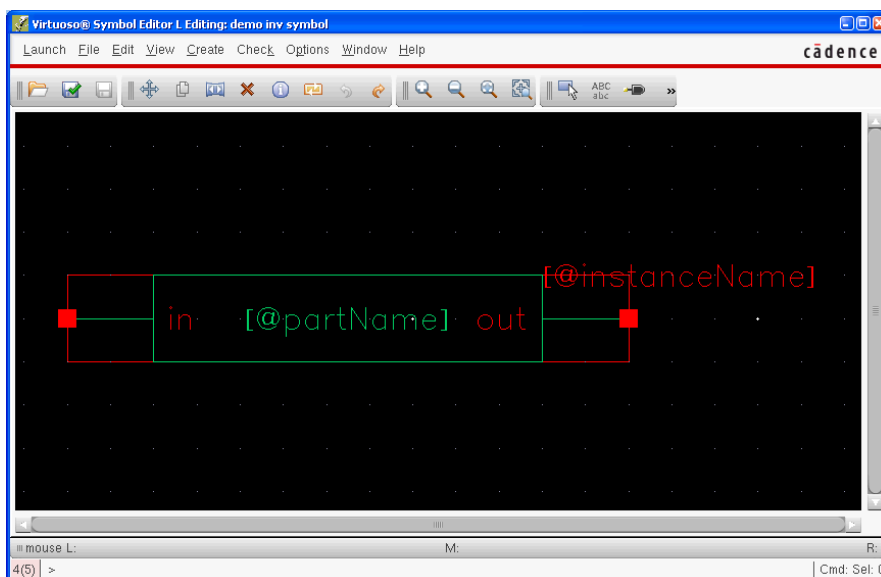

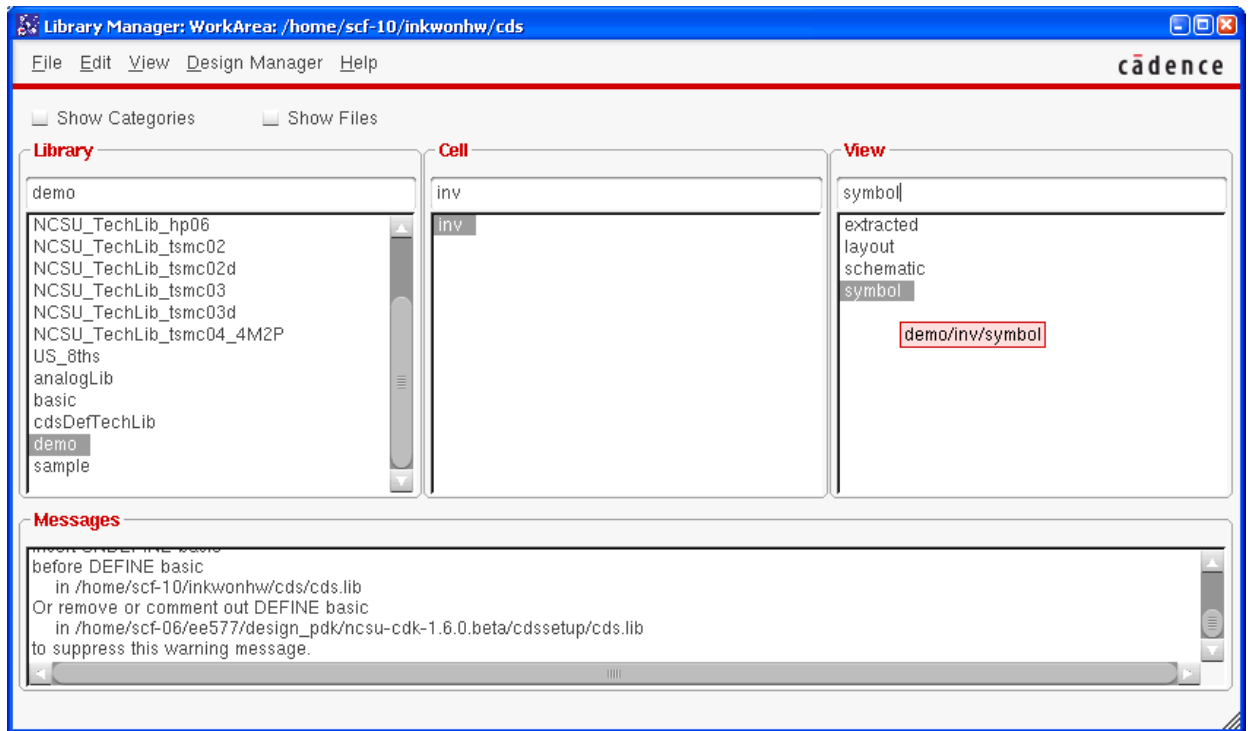


Remember that when you use more than one symbol in schematic, they all will have common Vdd and Gnd even if there are one Gnd and Vdd for each symbol (in the original design). To design with symbols in layout, you should make sure that all of the Vdd and Gnds are connected.

4. Run Spectre simulation (Transient analysis)

We will run spectre simulation. This section is for **both** schematics and layouts. I will show an example for a schematic. You can do the same thing for a layout.



A. Launch ADE (Analog Design Environment) L

Launch → ADE L

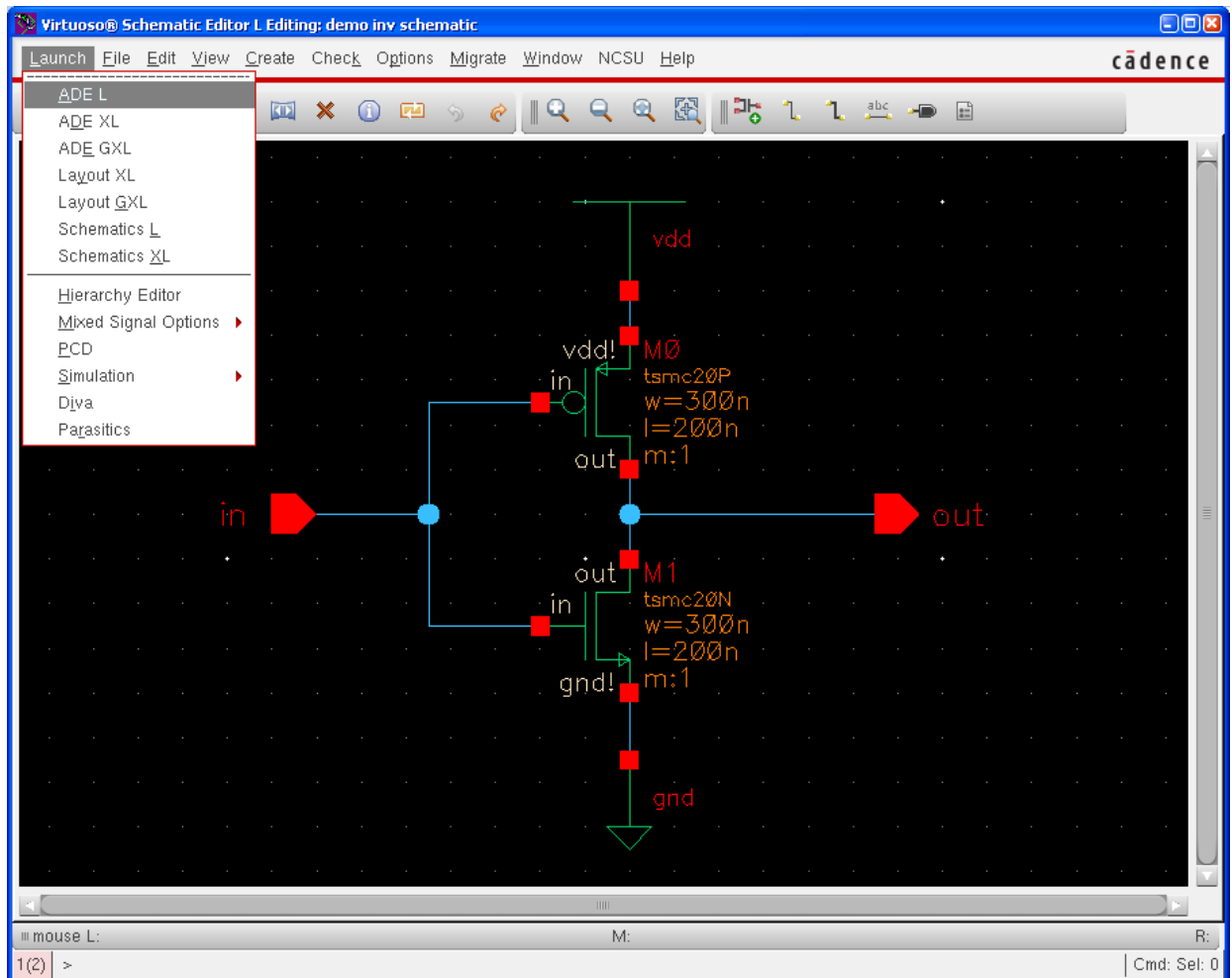

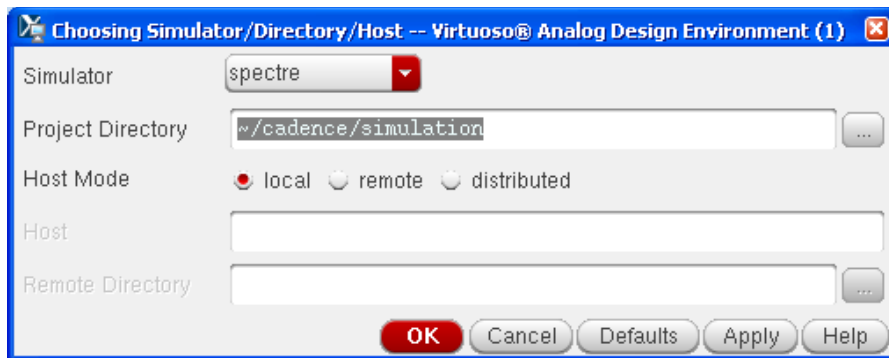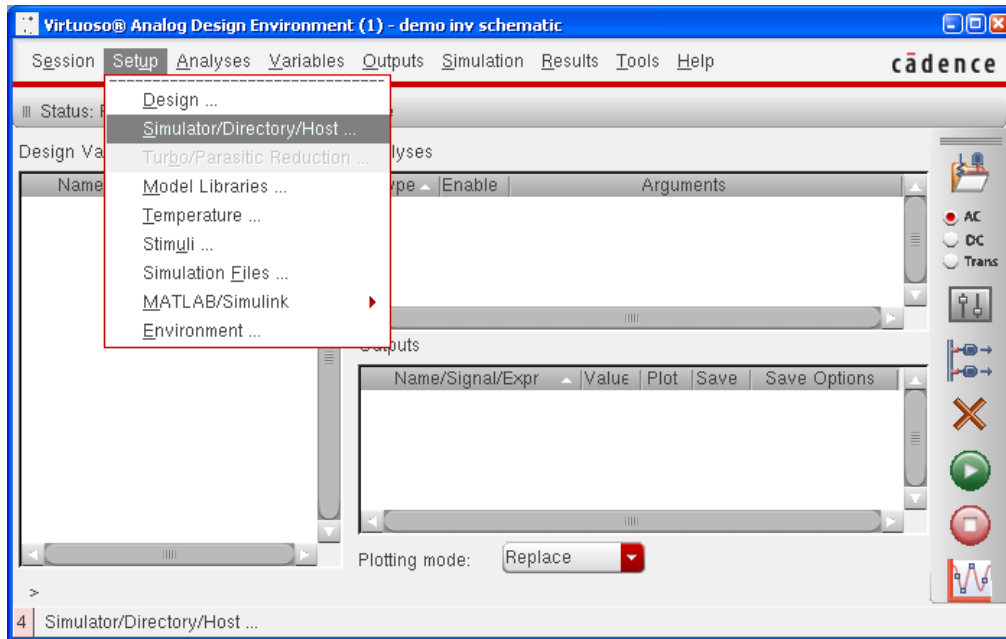B. Basic setup


Check if your simulator is spectre. You can modify project directory.




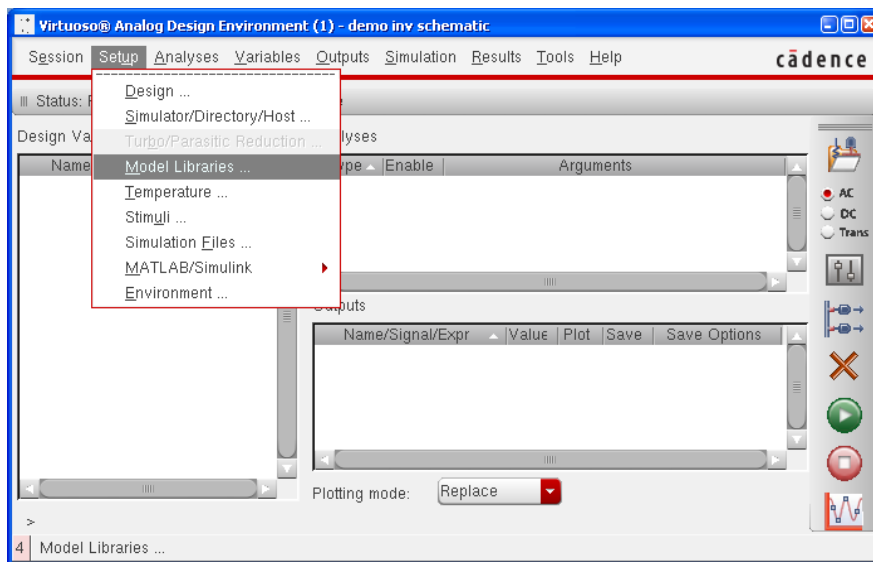C. Model Libraries

You can download a library file at the DEN blackboard.

Put the tech file under /home/scf-10/your-user-name/cds/techfiles/




 

Please only use the provided tsmc file because some tsmc files does not work correctly.

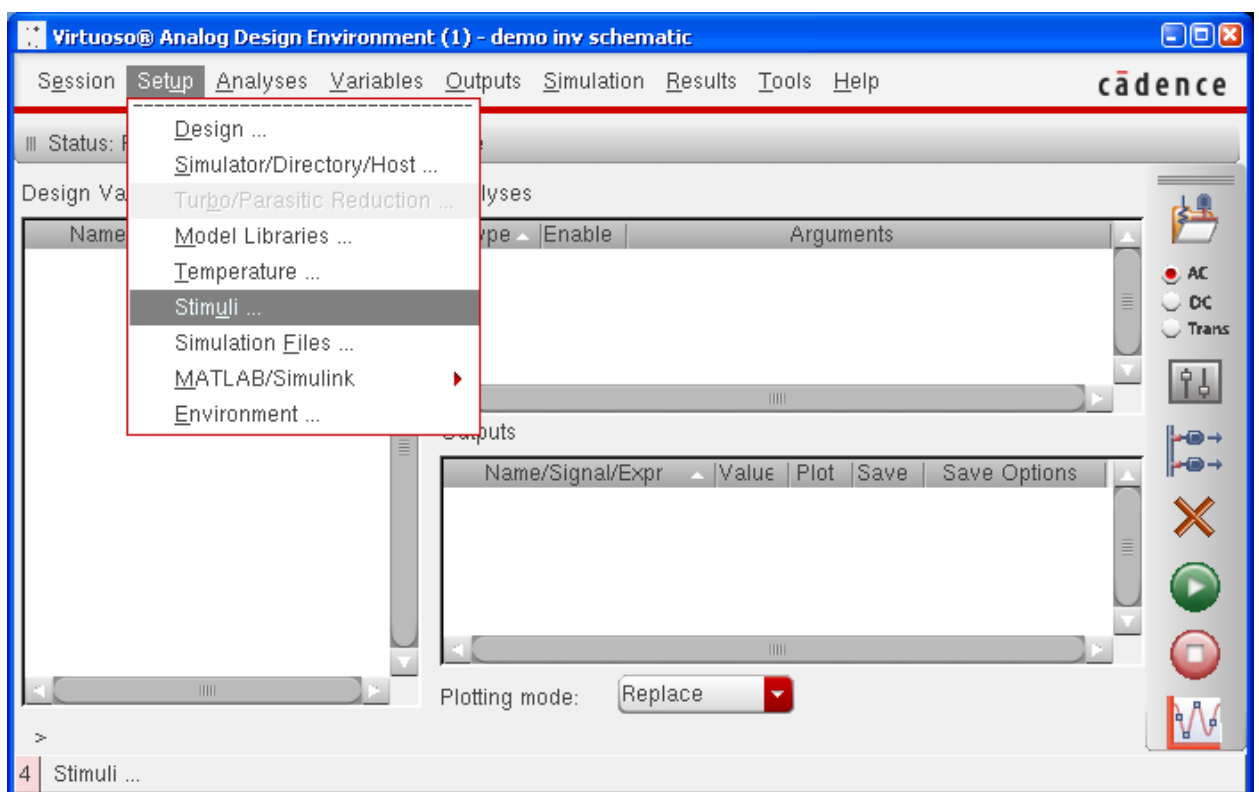D. Stimuli

Define input signals include supply nets (for layout, vdd! and gnd! are under inputs and both should be enabled.)



Global sources

Setup Analog Stimuli

Stimulus Type: ☐ Inputs ☒ Global Sources

ON vdd! /gnd! Voltage dc "DC voltage"=1.5

Enabled ☒ Function: dc Type: Voltage

DC voltage: 1.5

AC magnitude:

AC phase:

XF magnitude:

PAC magnitude:

PAC phase:

Temperature coefficient 1:

Temperature coefficient 2:

Nominal temperature:

Source type: dc

Noise file name:

Number of noise/freq pairs: 0

Freq 1:

Noise 1:

Freq 2:

Noise 2:

Freq 3:

OK Cancel Apply

Input (change)

Setup Analog Stimuli

Stimulus Type: ☒ Inputs ☐ Global Sources

ON in /gnd! Voltage pulse "Voltage 1"=0 "Voltage 2"=1.5

Enabled ☒ Function: pulse Type: Voltage

DC voltage:

AC magnitude:

AC phase:

XF magnitude:

PAC magnitude:

PAC phase:

Voltage 1: 0

Voltage 2: 1.5

Period: 2n

Delay time: 0

Rise time: 200p

Fall time: 200p

Pulse width: 1n

Temperature coefficient 1:

Temperature coefficient 2:

Nominal temperature:


Source type: pulse

OK Cancel Apply


Remember to check Enabled button and then press OK or APPLY otherwise you will lose the configured numbers.

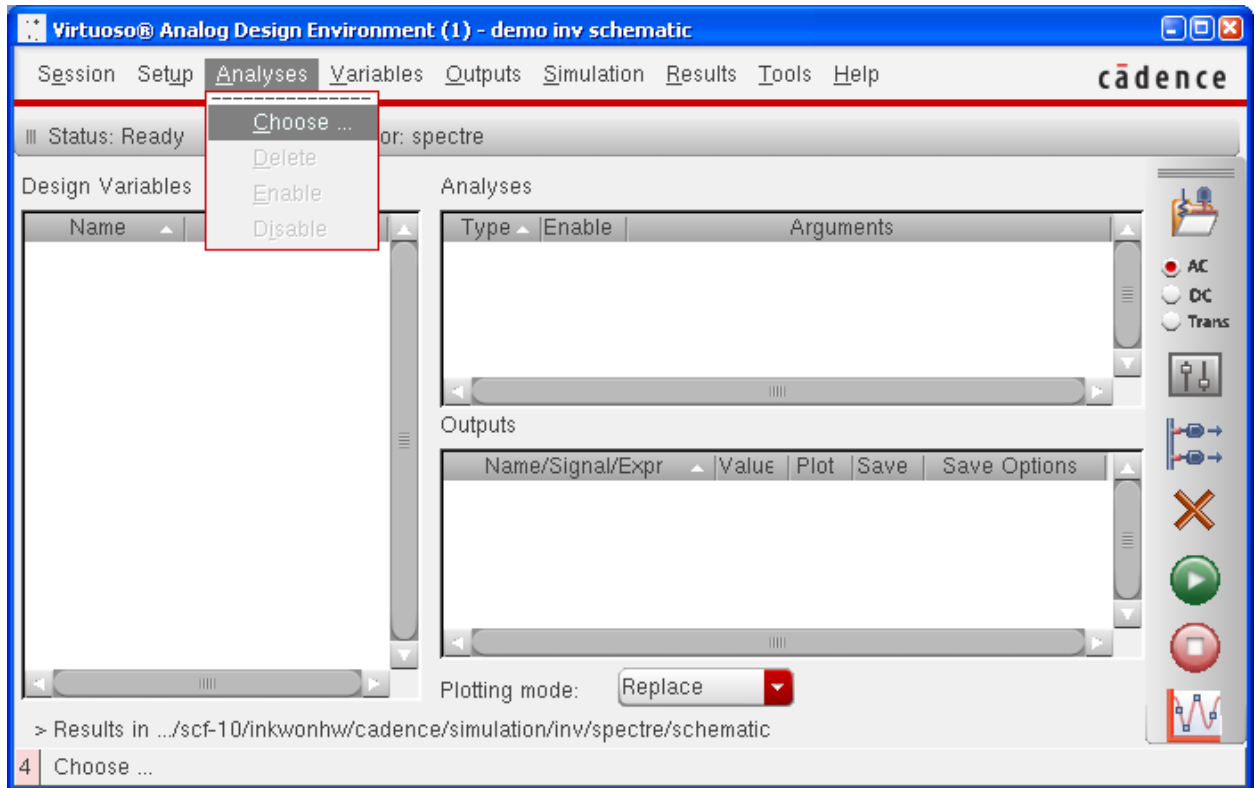E. Choose a type of analysis - transient

You can choose „dc“ if you want to do dc analysis



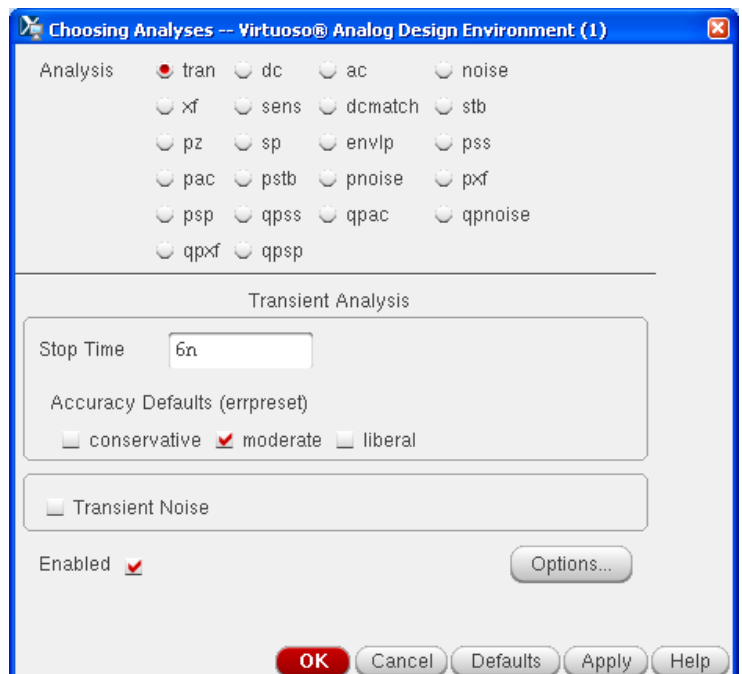
- A. Choose tran
- B. Give Stop time which means how long you want to simulate
- C. Select moderate as accuracy defaults
- D. Do not check Transient Noise
- E. Check Enabled



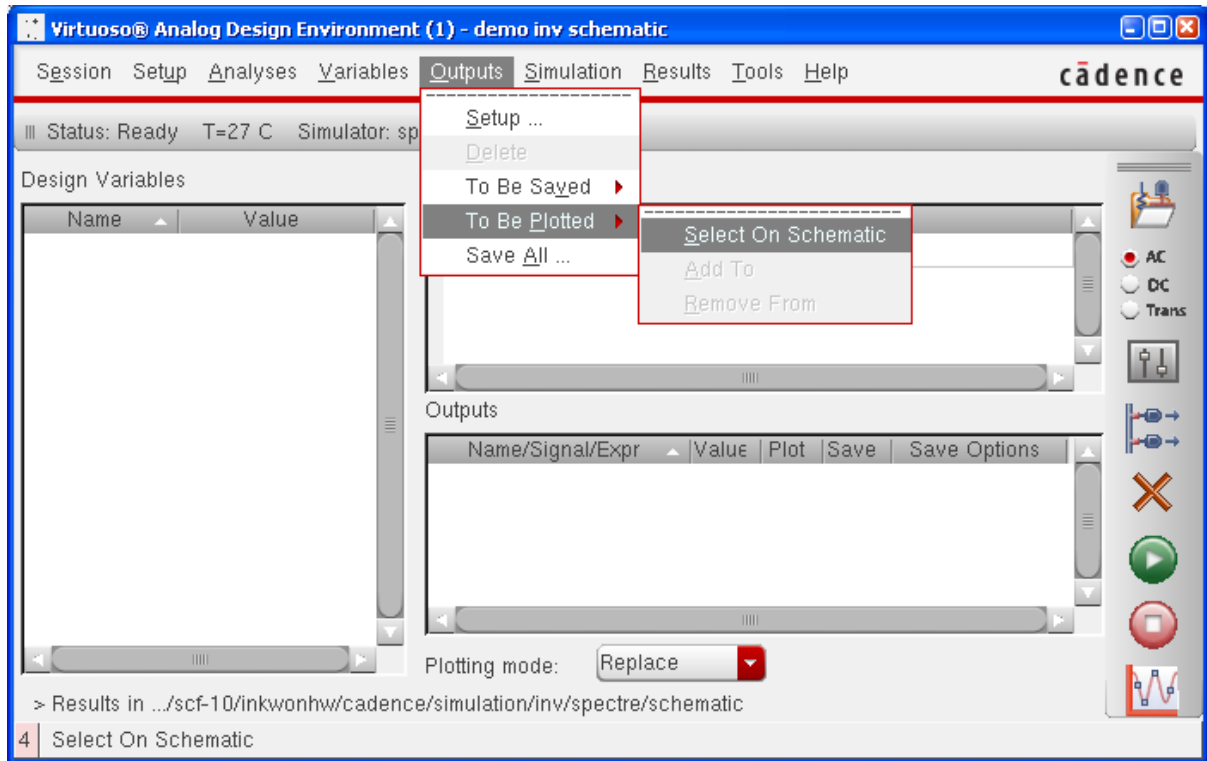F. Select signals to plot


Outputs → To Be Plotted → Select On Schematic


Click a signal (Pin) on a schematic/extracted. In Extracted try to use pins for signal that you need in the simulation because it is hard to select a net in the extracted view.



G. Run simulation

Simulation → Run

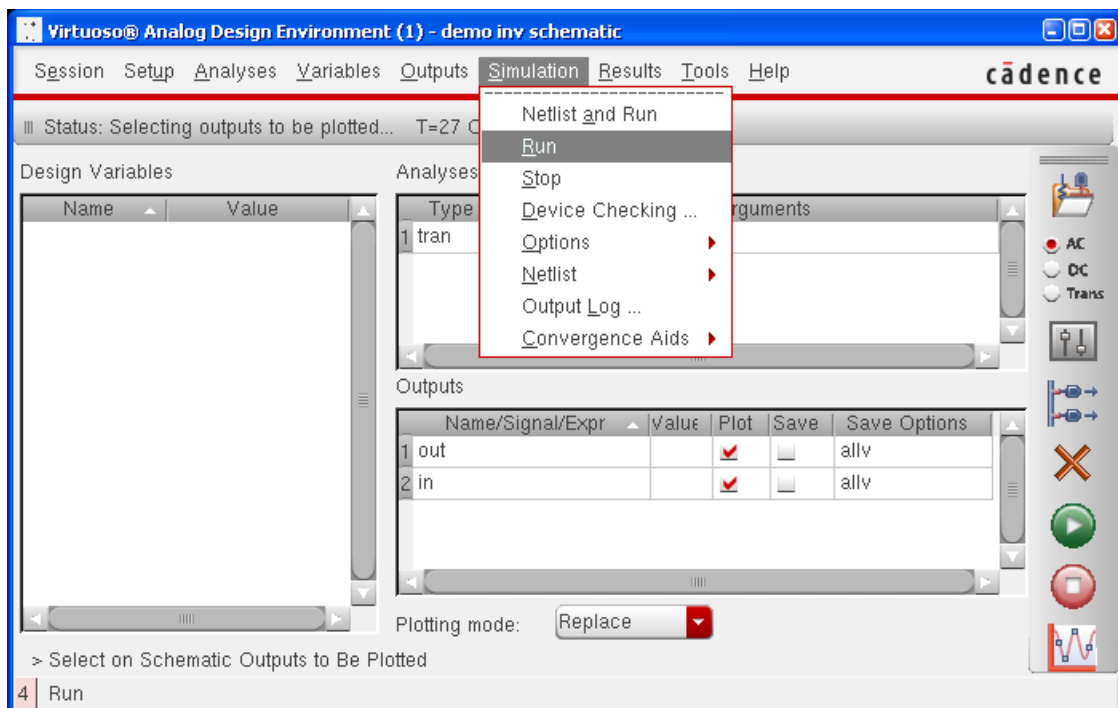

 
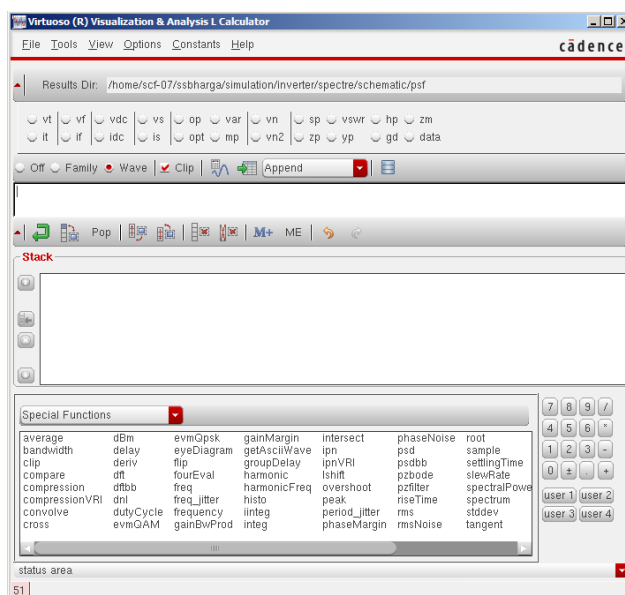



If you see a waveform like above picture, you followed every step properly.
Good job!.

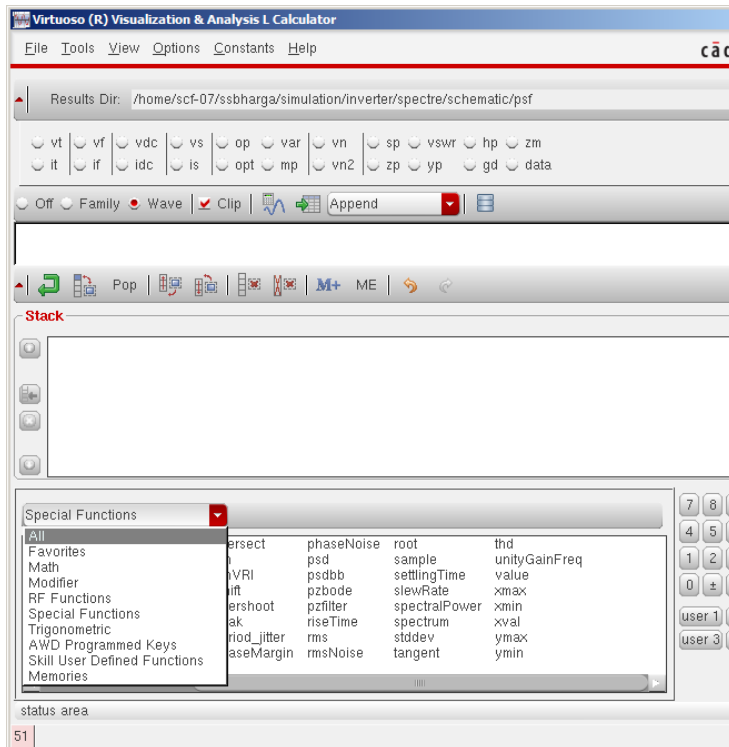H. Measurement


The following steps describe the measurement of rise time. Using similar steps other parameters of delay, fall time can be estimated.

Invoke the calculator  or tools-> calculator , select the Wave radio button:







In the functions window – choose “all”

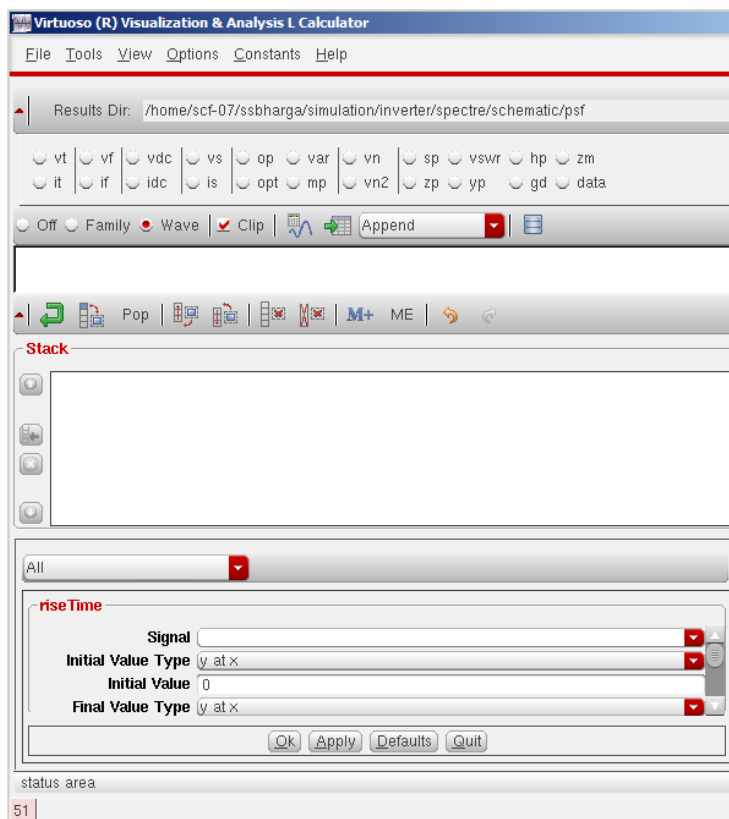

Select the rise time option

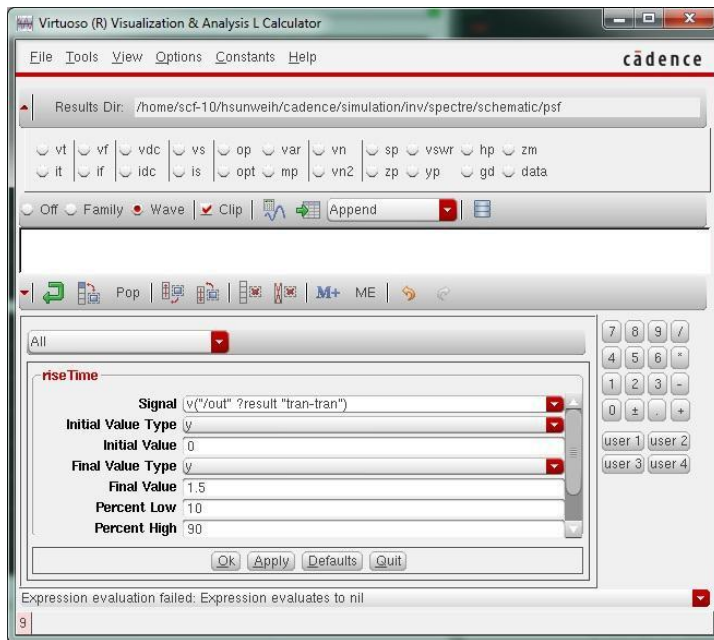

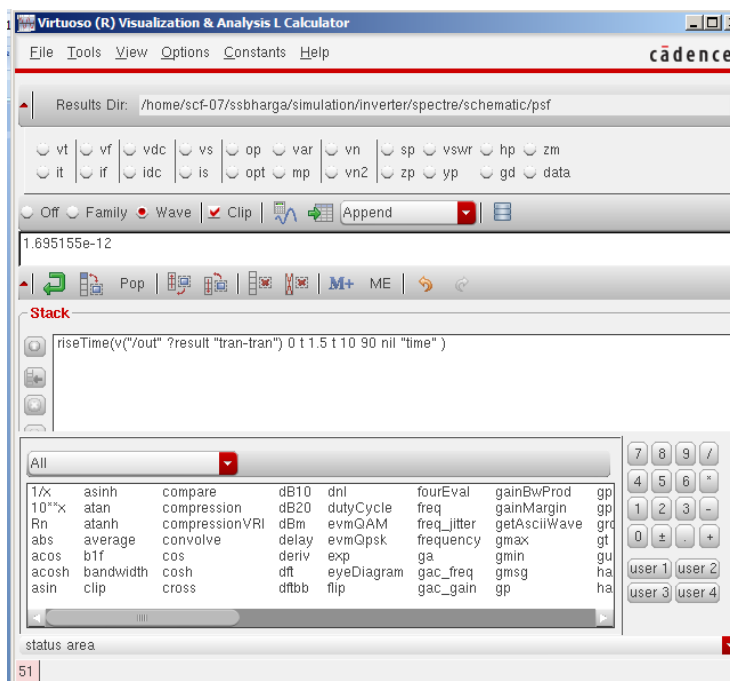Select the signal from the waveform window whose rise time needs to be determined and click “OK”:



Click the evaluate buffer → to display results as follows




You can also select a signal from calculator for example $\cos(V_{in})$ as one of the plotted signals and you can see the results whenever you run the simulation.

Remember to save the simulation setup to use it later. You can do so by clicking on **Session** → **Save State** in the ADE (Analog Design Environment) window. Next time you want to simulate the same cell, you can reload your configuration by clicking on **Session** → **Load State**.

 
5. Run Spectre simulation (DC analysis)

The following inverter schematic is already created



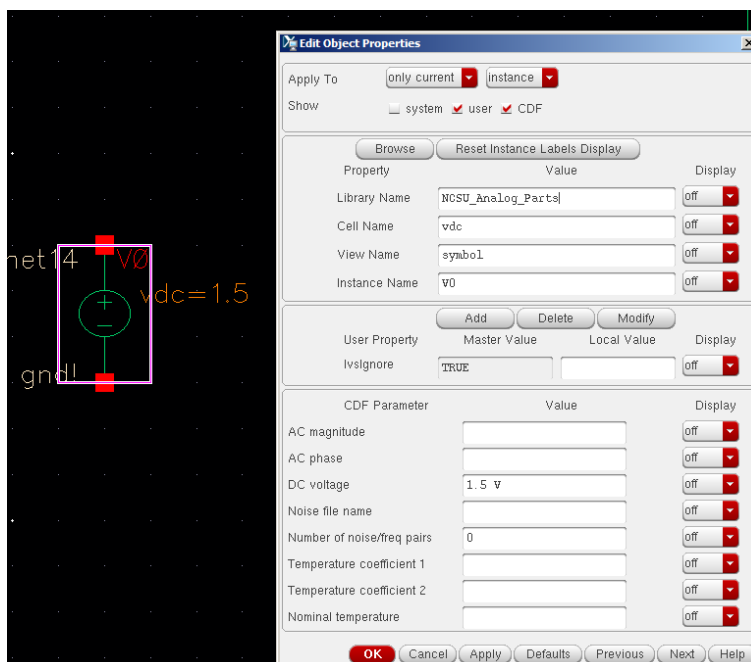A. Voltage Source


For DC analysis, the input pin “in” must be altered. The following are the steps to alter the pin “in”: Create→instance→NCSU analog parts→Voltage_sources select Vdc



The DC voltage must be set to 1.5V as shown.

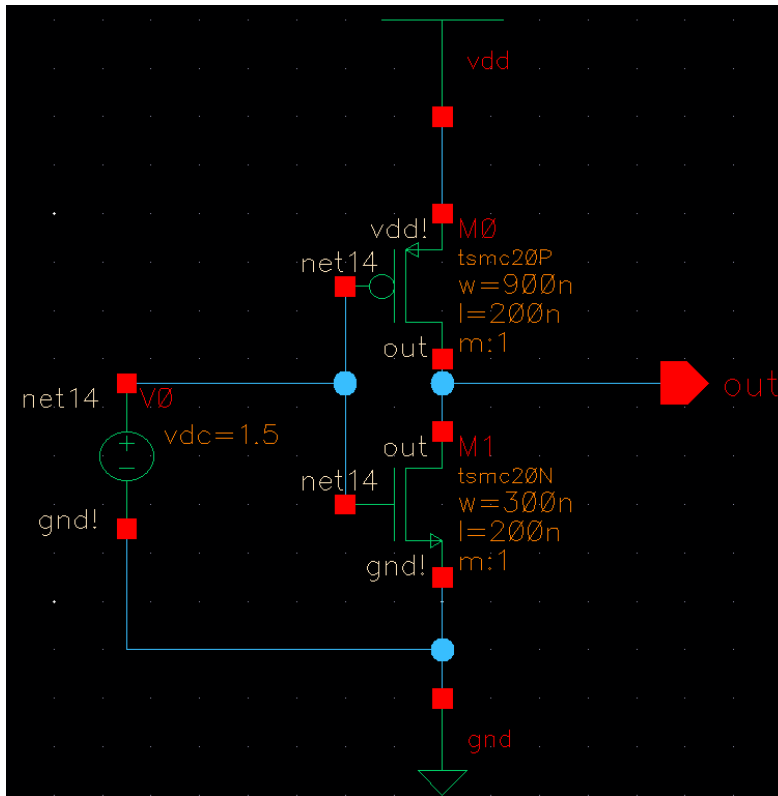B. Replace Input Pin


The Input pin “in” must be replaced with the above voltage source as shown below



Check and Save (make sure you get no errors)

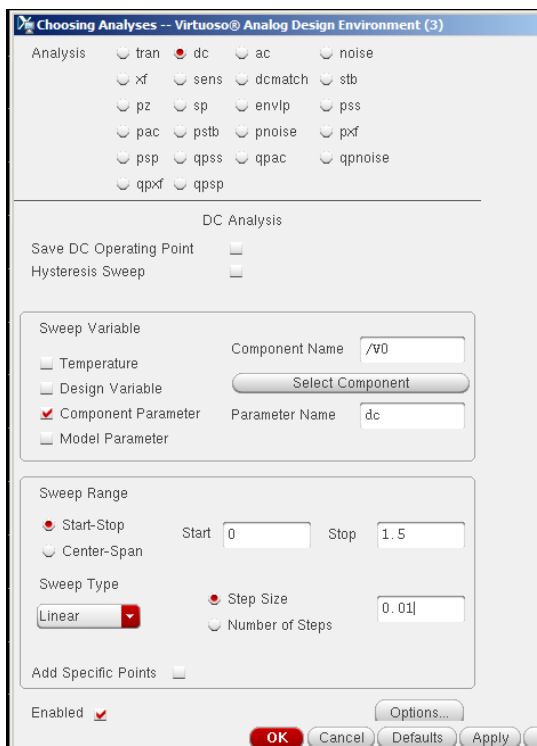C. Choosing Analyses

Launch ADE L, repeat steps A to D in section 3 of „Basic Design Flow“ except that there is no “in” input signal this time.




Go to Analyses → Choose dc

Choose „Component Parameter“,


Select Component, then the voltage source in the schematic, then choose 0 as Start, 1.5 as Stop and 0.01 as step .

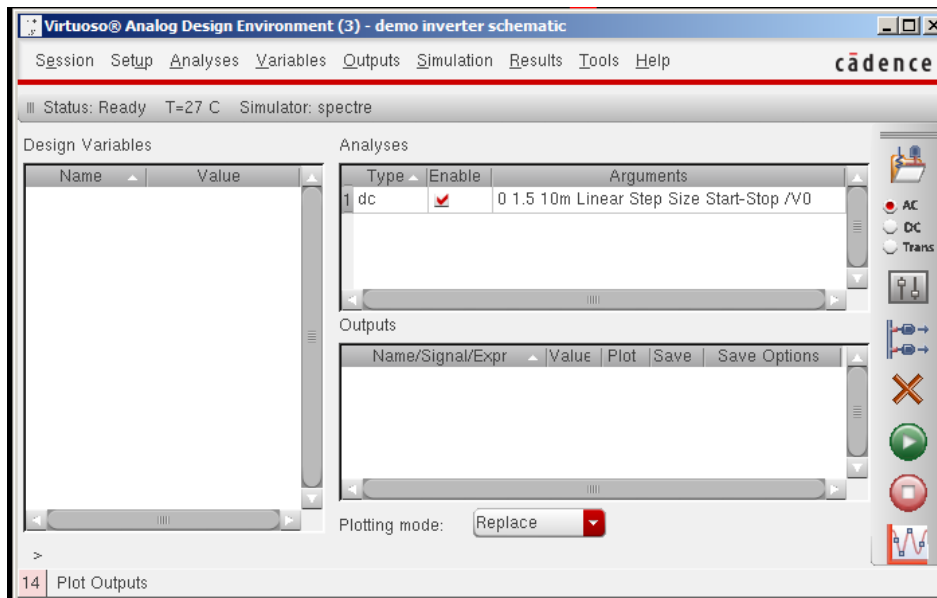Make sure that there are no other analyses selected apart from DC




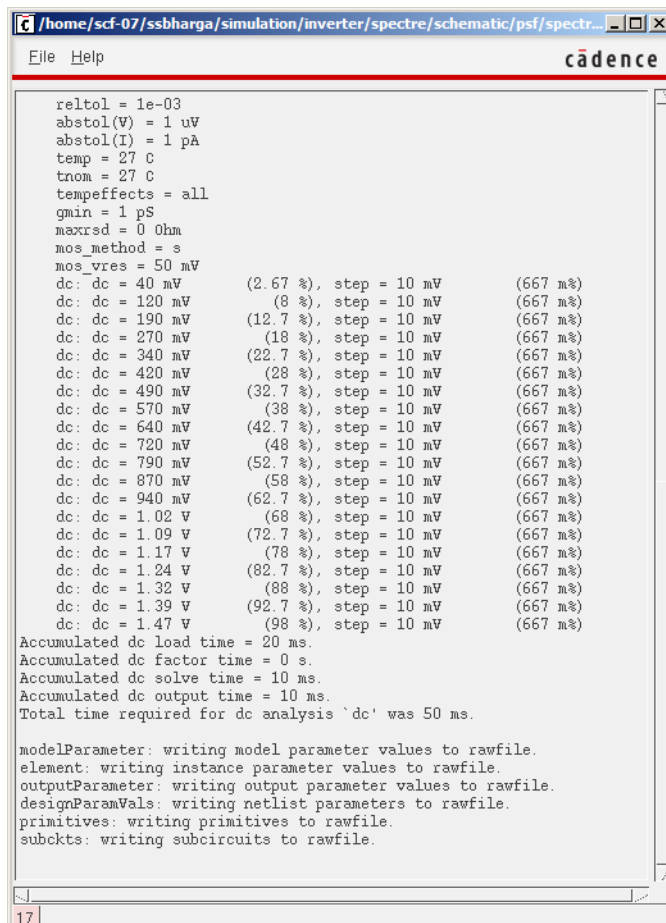D. Run Simulation

Do simulations → netlist and run. On successful completion we get the following



 Now, go to the results→Direct plot→DC. Click on the output pin “out” on the schematic and ESC key to get the following VTC




6. Layout

It's time to draw layout. Schematics are for verifying your design very roughly. They don't consider physical features like parasitic capacitances. After determining your design variables by schematics, you need to draw layouts.

Design flow of layouts is very similar to one of schematics, but it has additional step which is LVS check. It is for check if your layout is identical to the schematic or not. Hence, this step is very important. If your logic doesn't pass this step, you may lose significant points for that.

A. Create a layout

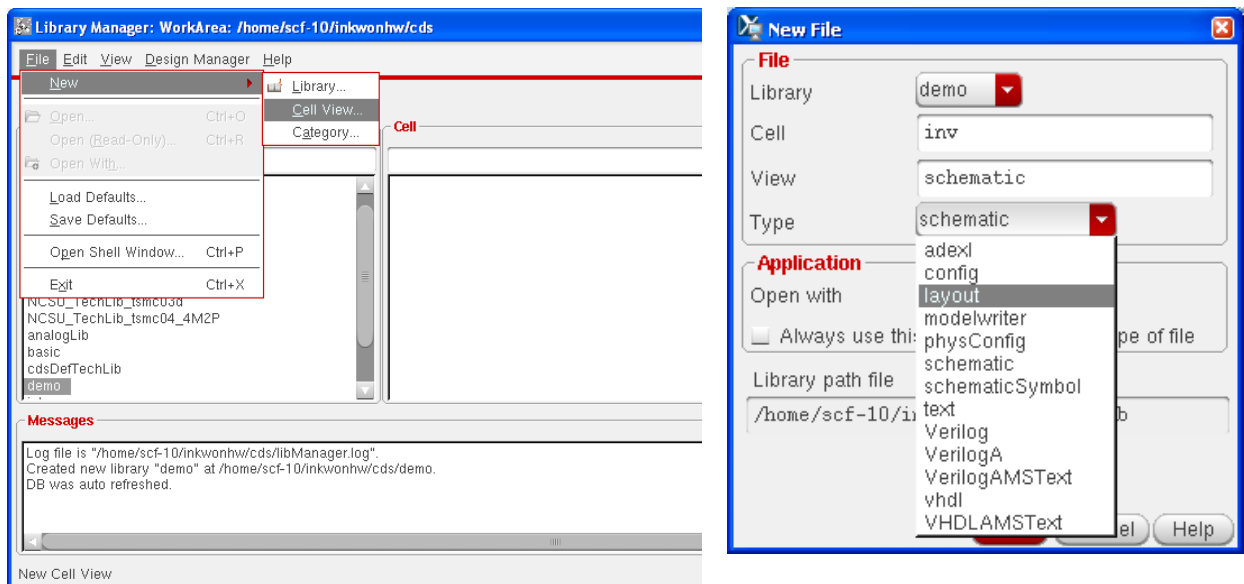

B. Add an instance - nmos

The image shows two windows from the Virtuoso Layout Suite L. The top window is the 'Create Instance' dialog, and the bottom window is the 'Library Browser - Create Instance' window.

Create Instance Dialog:


- Library: NCSU_TechLib_tsmc02
- Cell: nmos
- View: layout
- Names: I1
- Mosaic: Rows 1, Columns 1, Delta Y 0.8, Delta X 1.6
- Halo: ☒ Define Halo ...
- Physical Only: ☐
- Buttons: Rotate, Sideways, Upside
- Model name: tsmc20N
- Model Type: ☒ system ☐ user
- Multiplier: 1
- Fingers: 1
- Width (grid units): 6
- Width: 300n M
- Width (minimum): 300n M
- Length (grid units): 4
- Length: 200n M
- Length (minimum): 200n M
- Drain diffusion area: 1.5e-13
- Source diffusion area: 1.5e-13
- Drain diffusion perimeter: 1.6u M
- Buttons: Hide, Cancel, Defaults

Library Browser - Create Instance:


- Show Categories: ☒
- Library: NCSU_TechLib_tsmc02
- Category: Everything
- Cell: nmos
- Buttons: Close, Filters...

You can modify width of transistors.

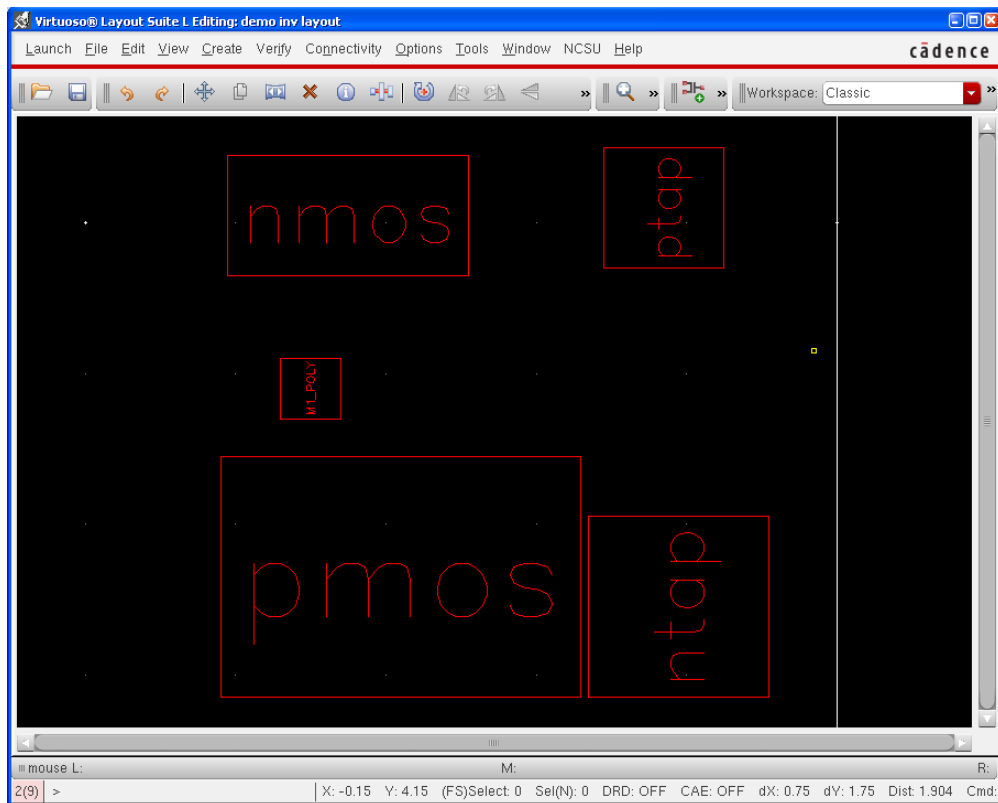C. Add more instances – pmos, ptap, ntap, and m1_ploy



 You can select alternate view of a layout. Try „Shift + f“ and „Ctrl + f“.




D. Draw metal1

There are few ways for drawing metal, but I recommend you use „path“. It's quite convenience than others.

Create → Shape → Path




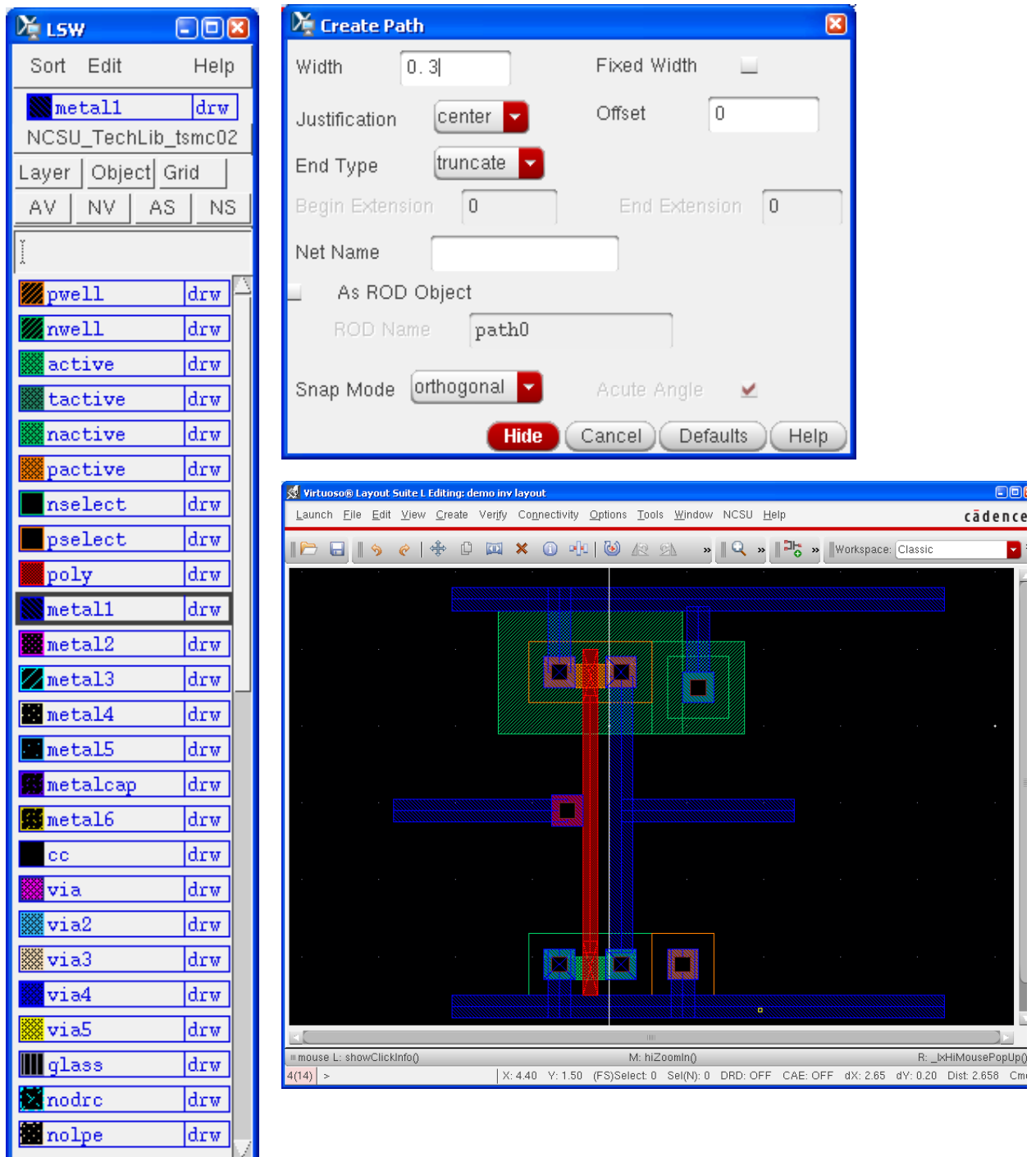
First of all, you should select metal1 on LSW window. Default width for metal1 is 0.3, which means 300nm (3λ). You can draw metal layer simply by clicking




E. Run DRC

This step checks if your layout follows design rules.

Verify → DRC

 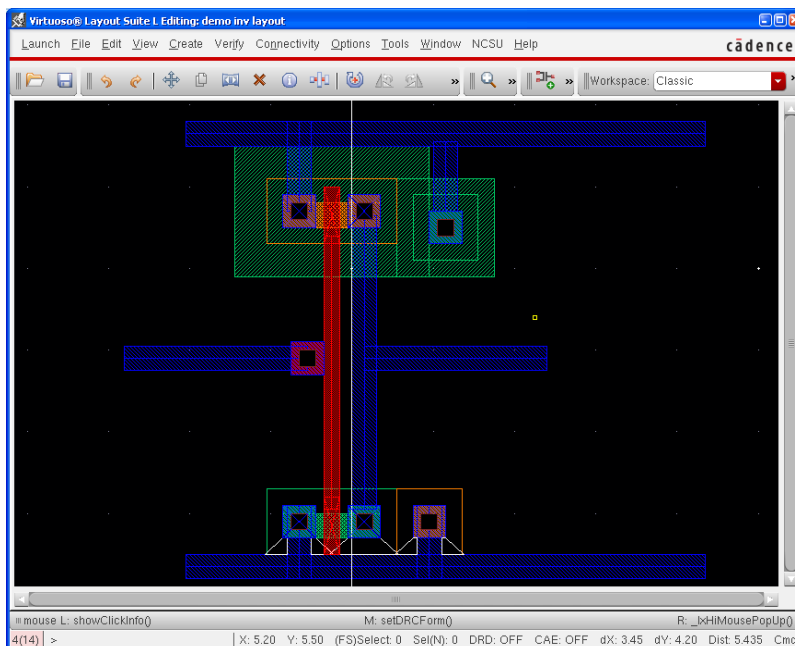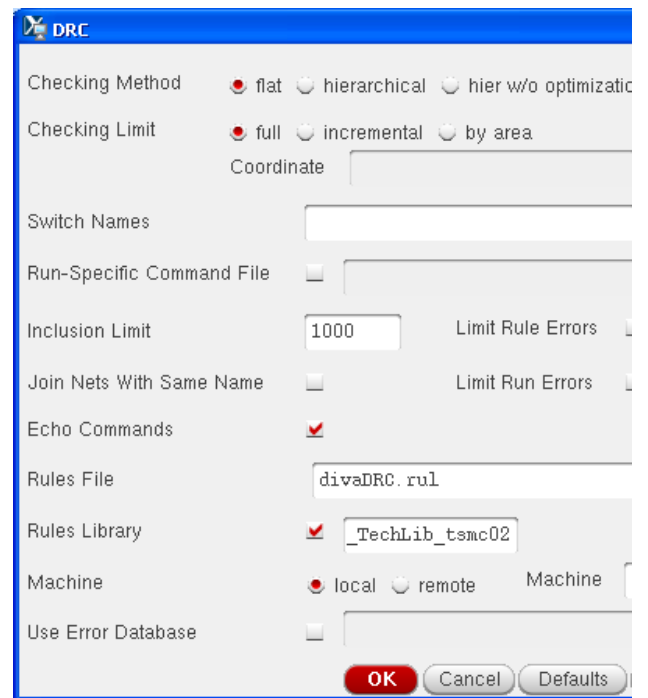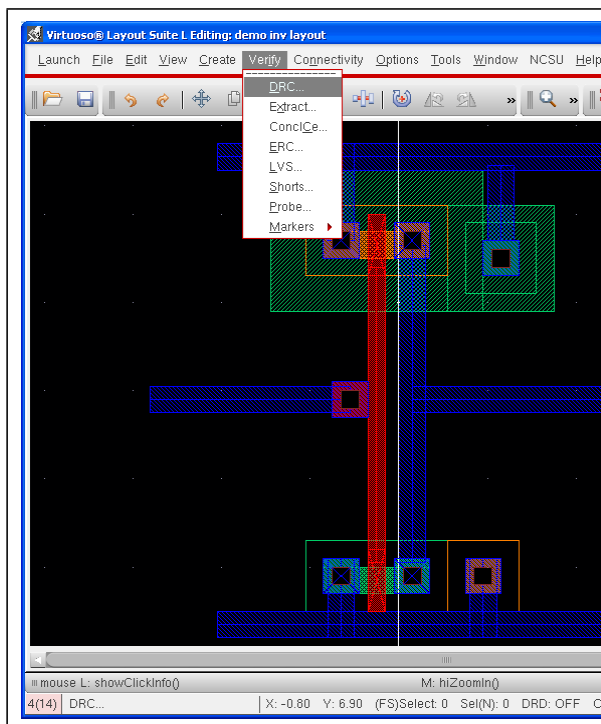

 We have five errors. It is because a gnd metal layer is too close to an nmos transistor.
After modifying layout, run DRC again.




There is no error!!

F. Add pins


We had two pins on a schematic, which are „in“ and „out“. Pins are for assigning signals to physical device, so we assign voltage level of gnd and vdd by using pins. Hence, we have 4 pins for the layout, which are „in“, „out“, „gnd!“, and „vdd!“.


Create → Pin

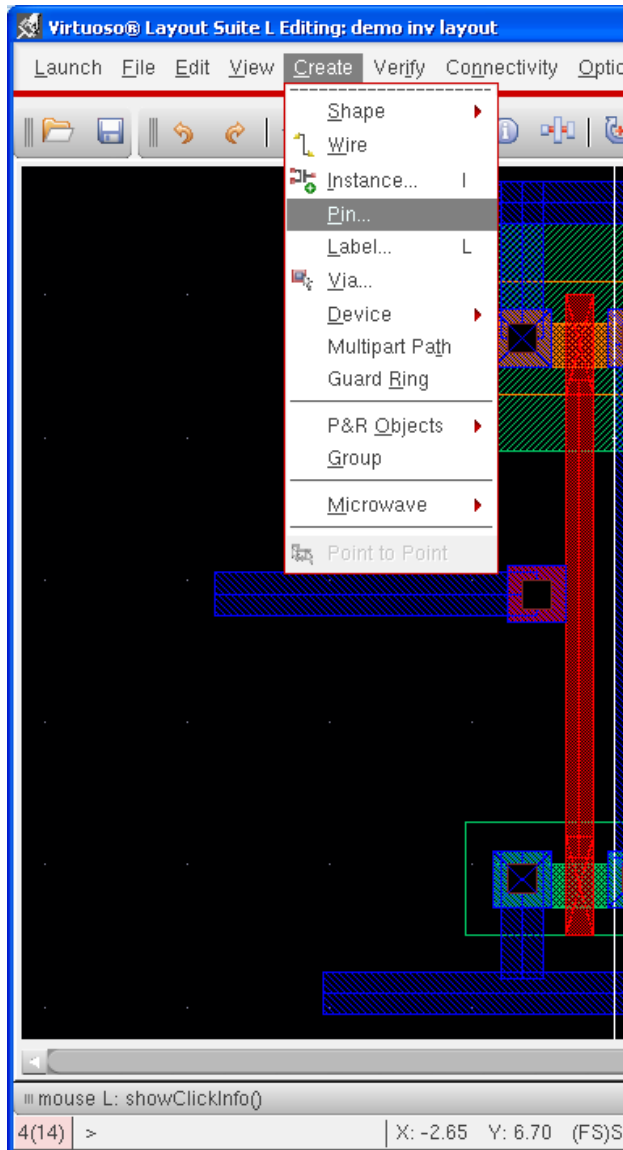

Check „Display Terminal Name“ if you want to see pin name on the layout.


Click „Display Terminal Option“

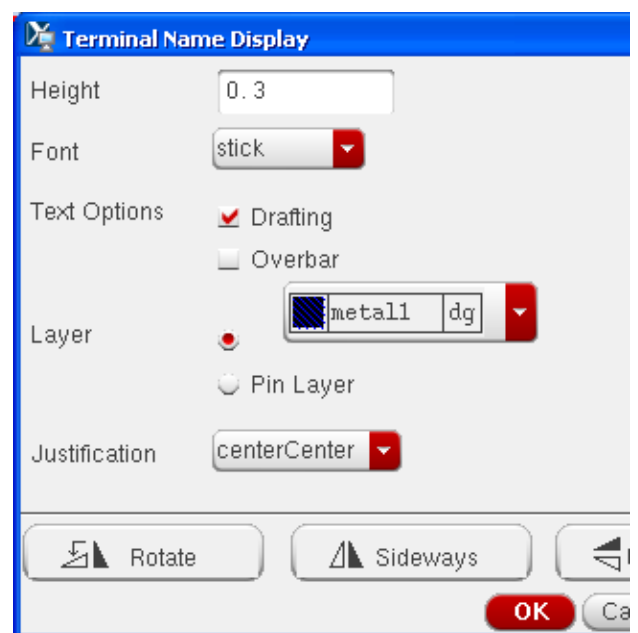

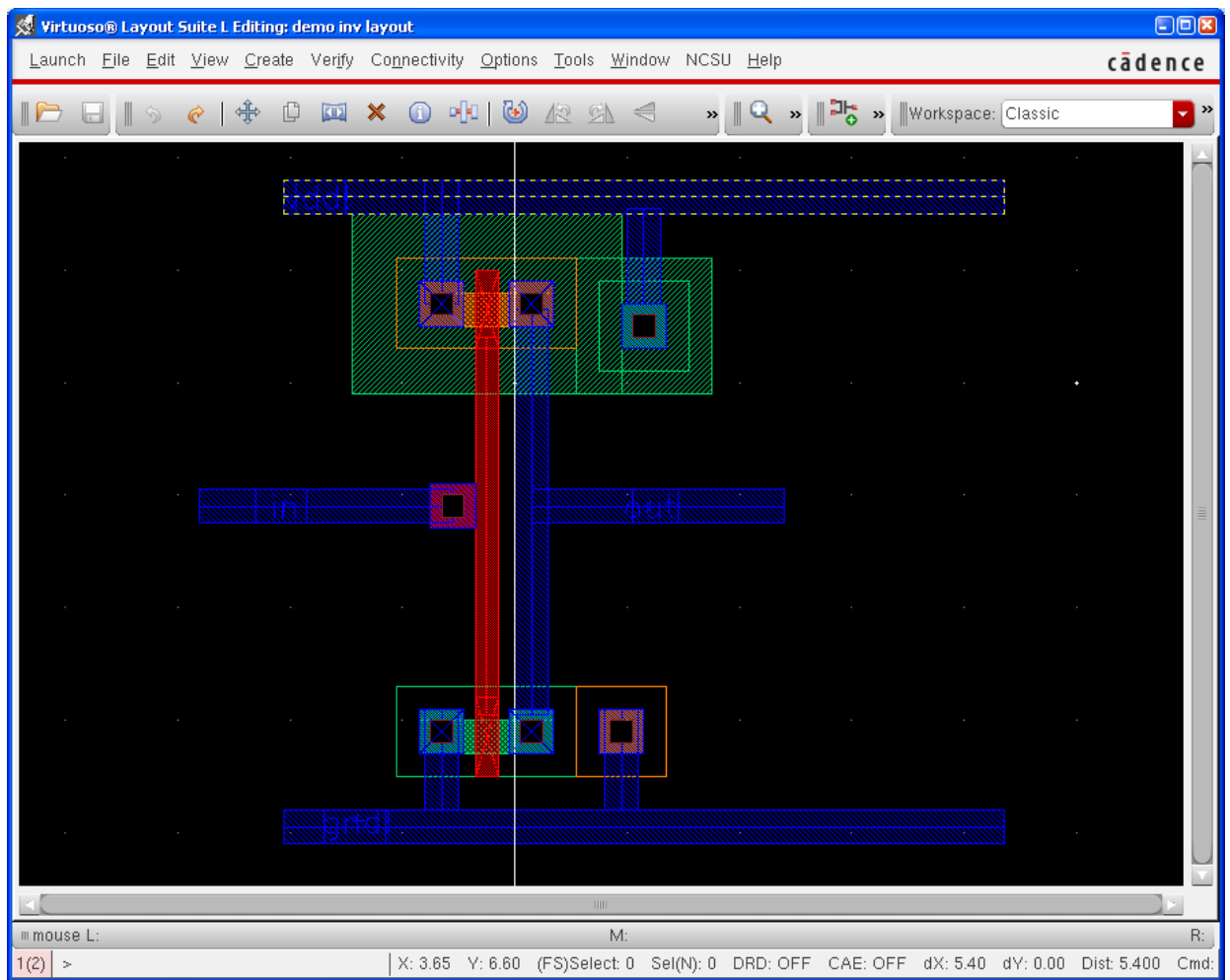


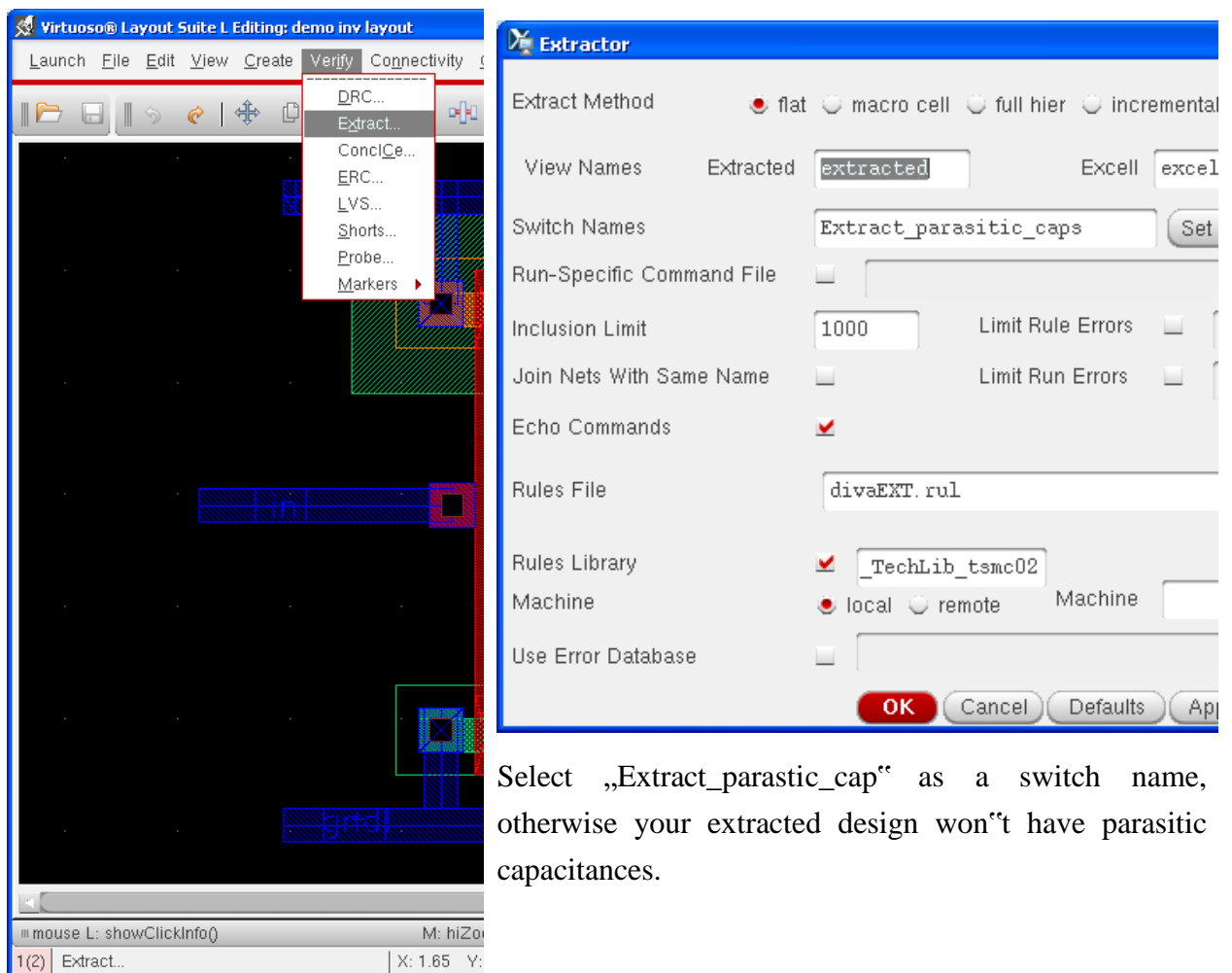G. Extract

A layout is just a picture. If you need to run simulation using the layout, you should convert it to the other format. It is done by extracting. It's something like compiling a code.



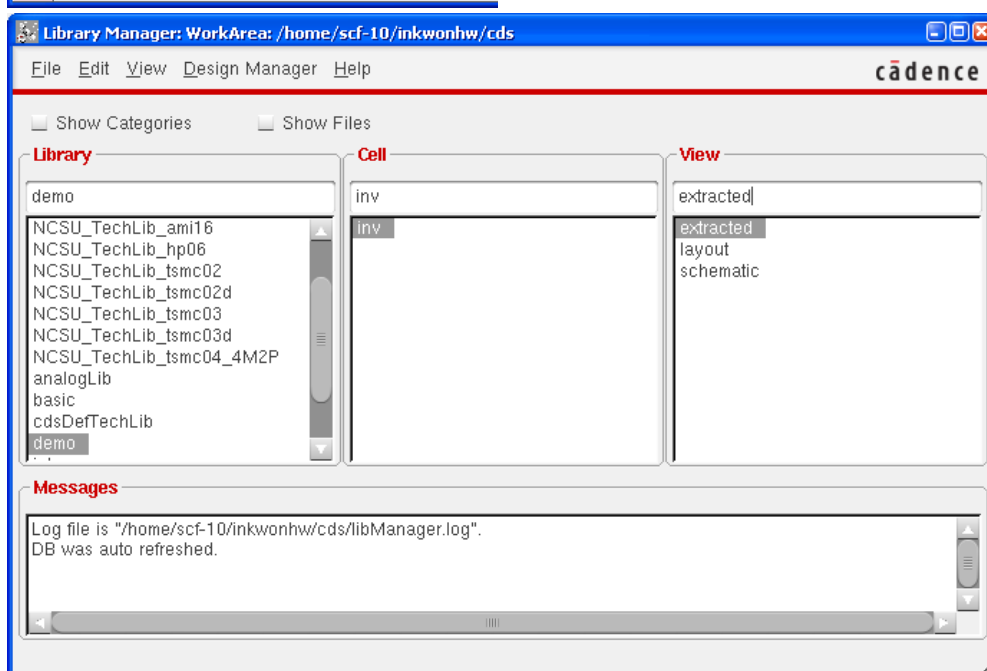Select „Extract_parastic_cap“ as a switch name, otherwise your extracted design won't have parasitic capacitances.




H. Run LVS


As I mentioned before, this step is very important for your grading. More complicated design, more time will be required for debugging LVS.

Verify → LVS

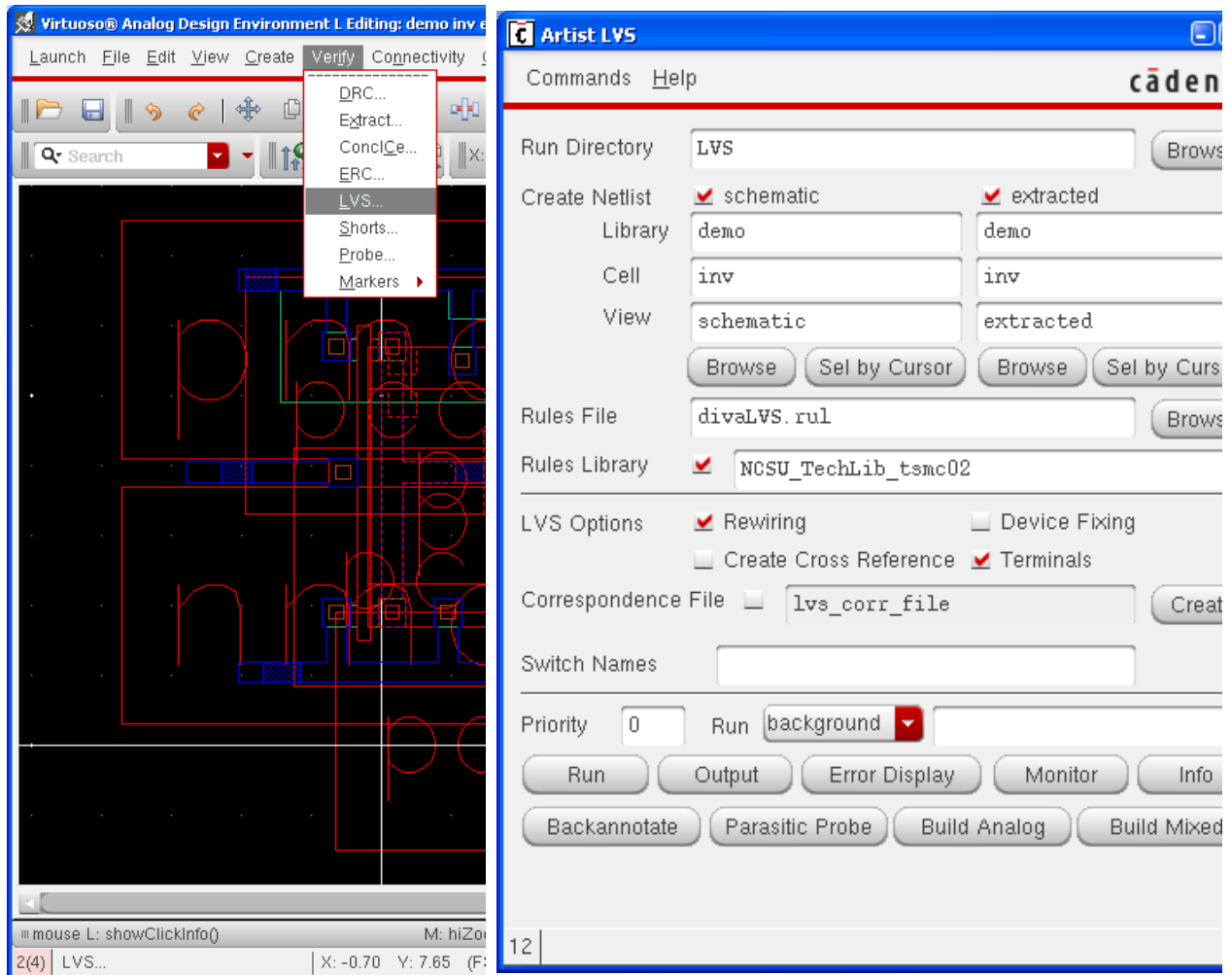Keep in mind. You **SHOULD** compare your schematic with **EXTRACTED**.




 
I hope all of you will see the following window.



If there are errors, you can check the results by clicking „Output“ button. „Error Display“ also might be helpful.

 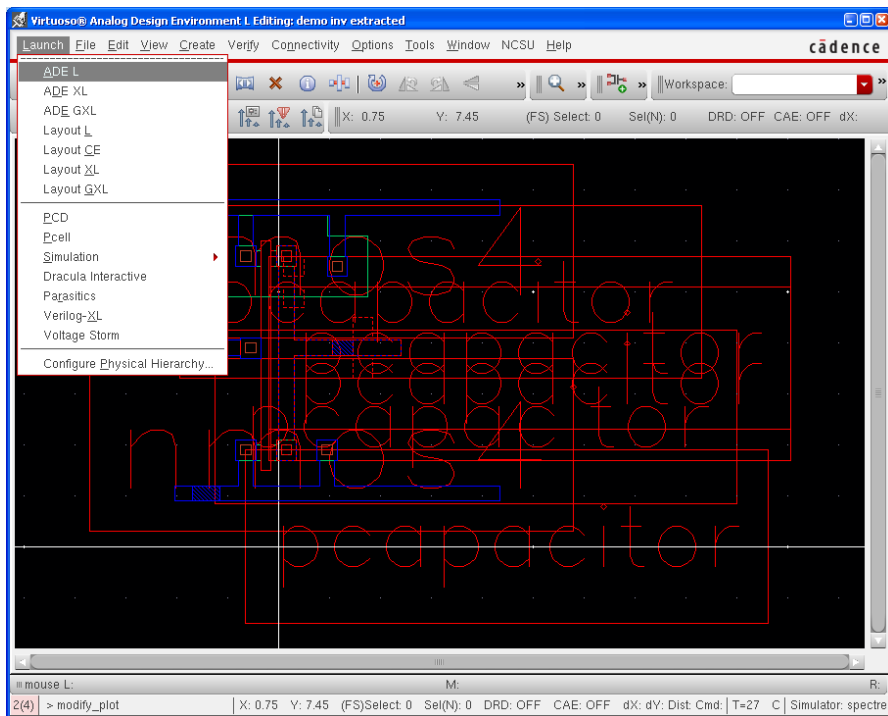I. Run Spectre simulation

It is same as schematics. Please follow the instructions for the schematics.



Congratulations!!

You followed all steps I prepared. Let's do the same thing for more complicated designs.

***Some useful information**

Useful Links:

<http://www.edaboard.com/>

[http://www.eda.ncsu.edu/wiki/NCSU_EDA_Wi](http://www.eda.ncsu.edu/wiki/NCSU_EDA_Wiki)

[ki](#)

[http://www.cadence.com/community/forum](http://www.cadence.com/community/forums/)

[s/](#)